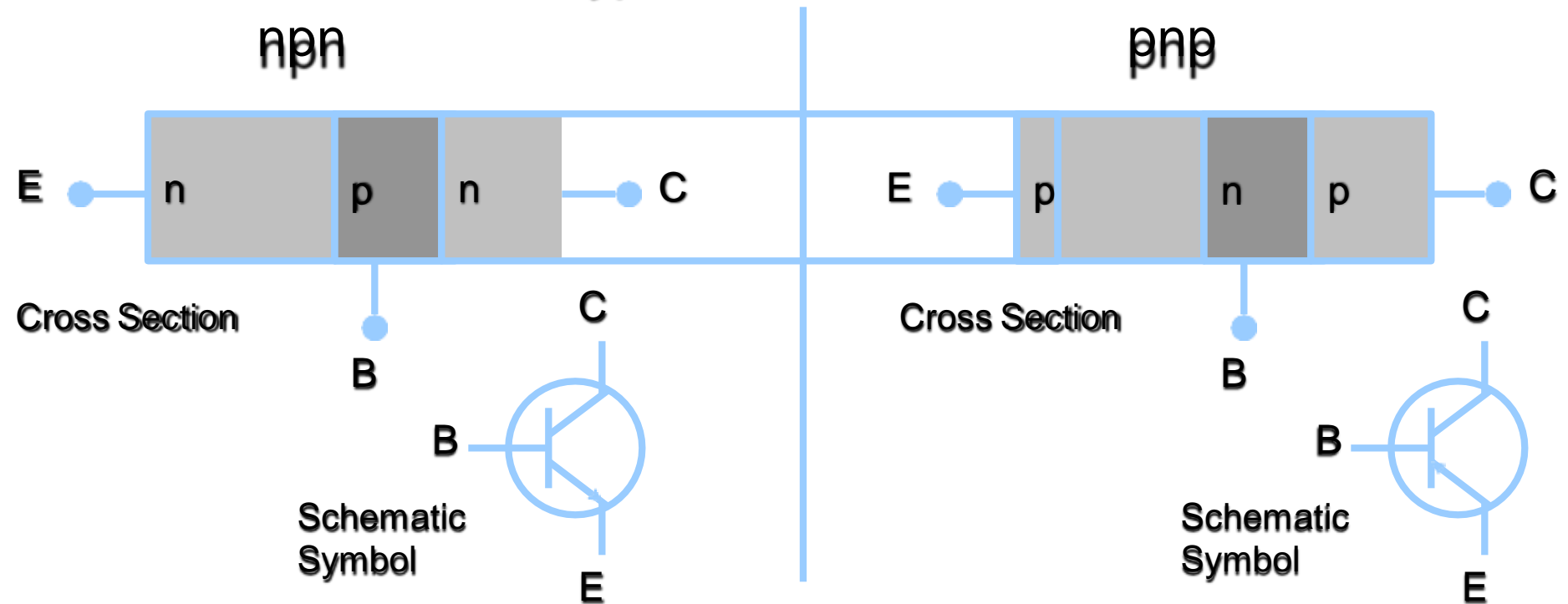


UNIT - V

BIPOLAR JUNCTION TRANSISTOR AND APPLICATIONS


The BJT – Bipolar Junction Transistor

The Two Types of BJT Transistors:



- Collector doping is usually $\sim 10^{16}$
- Base doping is slightly higher $\sim 10^{17} - 10^{18}$
- Emitter doping is much higher $\sim 10^{19}$


BJT Relationships - Equations

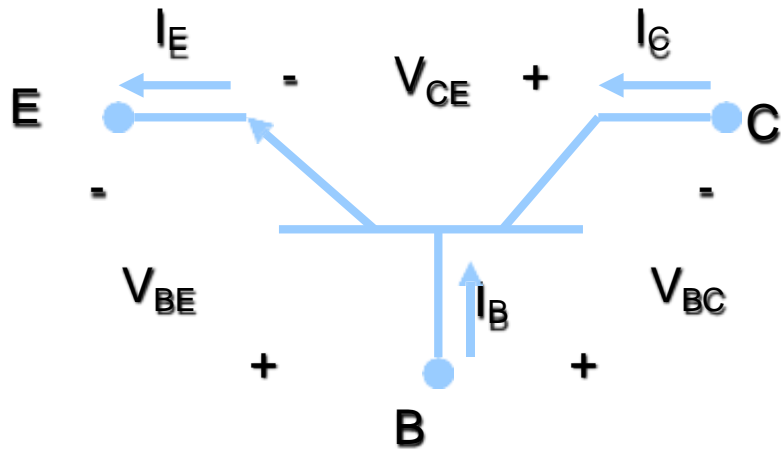

npn

$$I_E = I_B + I_C$$

$$V_{CE} = -V_{BC} + V_{BE}$$

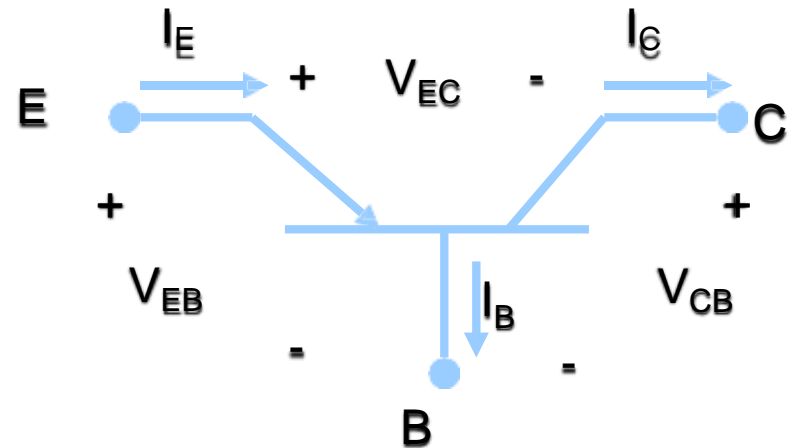

pnp

$$I_E = I_B + I_C$$

$$V_{EC} = V_{EB} - V_{CB}$$

Note: The equations seen above are for the transistor, not the circuit.

DC β and DC α

β = Common-emitter current gain

α = Common-base current gain

$$\beta = \frac{I_C}{I_B} \quad \alpha = \frac{I_C}{I_E}$$


The relationships between the two parameters are:

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha}$$

Note: α and β are sometimes referred to as α_{dc} and β_{dc} because the relationships being dealt with in the BJT are DC.

BJT Example

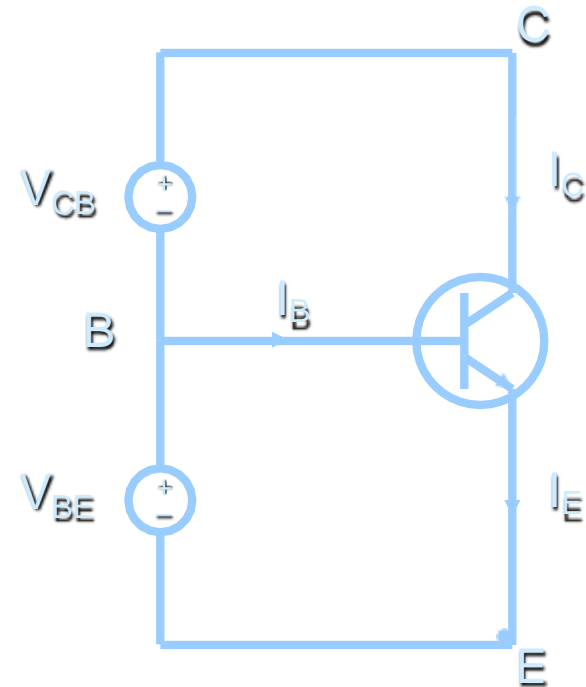Using Common-Base NPN Circuit Configuration



Given: $I_B = 50 \mu A$, $I_C = 1 \text{ mA}$

Find: I_E , β , and α

Solution:

$$I_E = I_B + I_C = 0.05 \text{ mA} + 1 \text{ mA} = 1.05 \text{ mA}$$

$$\beta = I_C / I_B = 1 \text{ mA} / 0.05 \text{ mA} = 20$$


$$\alpha = I_C / I_E = 1 \text{ mA} / 1.05 \text{ mA} = 0.95238$$

α could also be calculated using the value of β with the formula from the previous slide.

$$\alpha = \frac{\beta}{\beta + 1} = \frac{20}{21} = 0.95238$$

BJT Transconductance Curve

Typical NPN Transistor¹

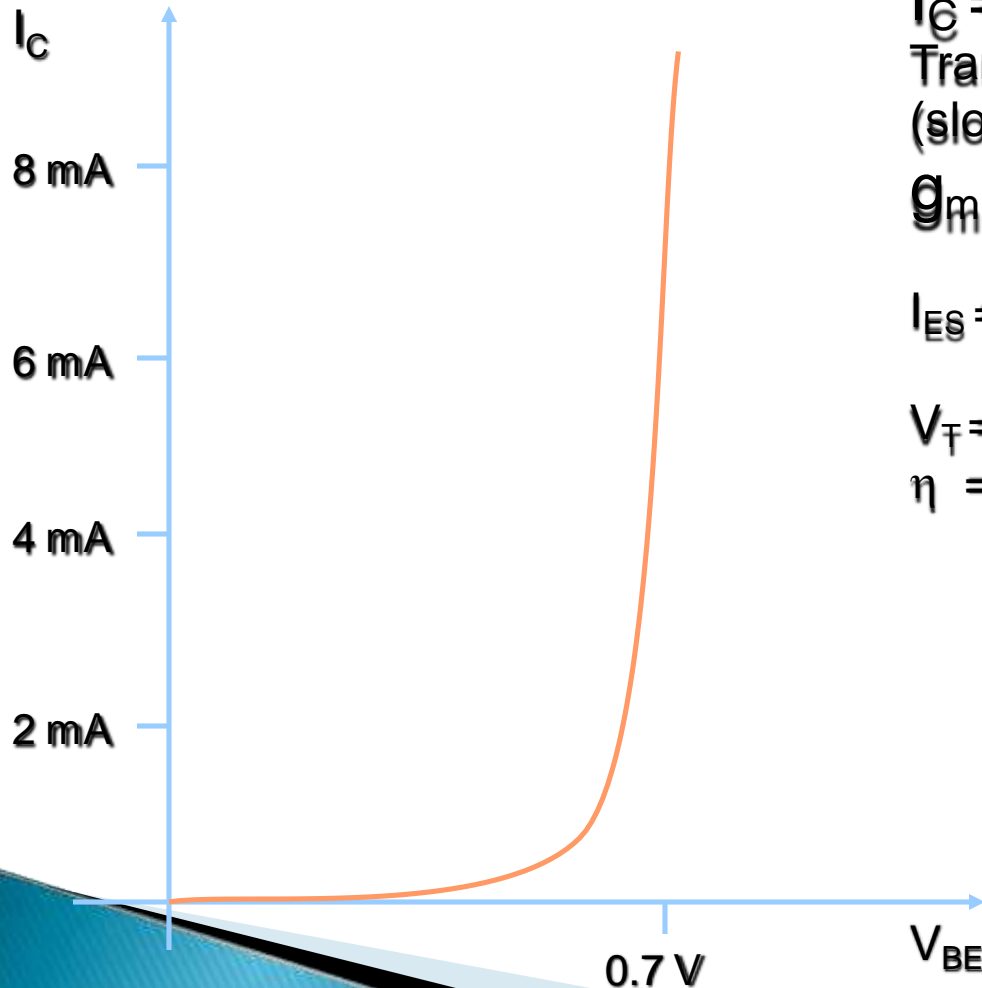

Collector Current:

$$I_C = \alpha I_{ES} e^{V_{BE}/\eta V_T}$$

Transconductance:
(slope of the curve)

$$g_m = \frac{dI_C}{dV_{BE}} = \frac{I_C}{V_{BE}}$$

I_{ES} = The reverse saturation current of the B-E Junction.

$$V_T = kT/q = 26 \text{ mV} \text{ (@ } T=300\text{K)}$$

η = the emission coefficient and is usually ~ 1

Modes of Operation

Active:

- Most important mode of operation
- Central to amplifier operation
- The region where current curves are practically flat

Saturation:

- Barrier potential of the junctions cancel each other out causing a virtual short

Cutoff:

- Current reduced to zero
- Ideal transistor behaves like an open switch

* Note: There is also a mode of operation called inverse active, but it is rarely used.

Three Types of BJT Biasing

Biasing the transistor refers to applying voltage to get the transistor to achieve certain operating conditions.

Common-Base Biasing (CB) : input $\equiv V_{EB} \& I_{E}$
 output $\equiv V_{CB} \& I_C$


Common-Emitter Biasing (CE) : input $\equiv V_{BE} \& I_B$
 output $\equiv V_{CE} \& I_C$

Common-Collector Biasing (CC) : input $= V_{BC} \& I_B$
 output $= V_{EC} \& I_E$

Common-Base


Although the Common-Base configuration is not the most common biasing type, it is often helpful in the understanding of how the BJT works.

Emitter-Current Curves

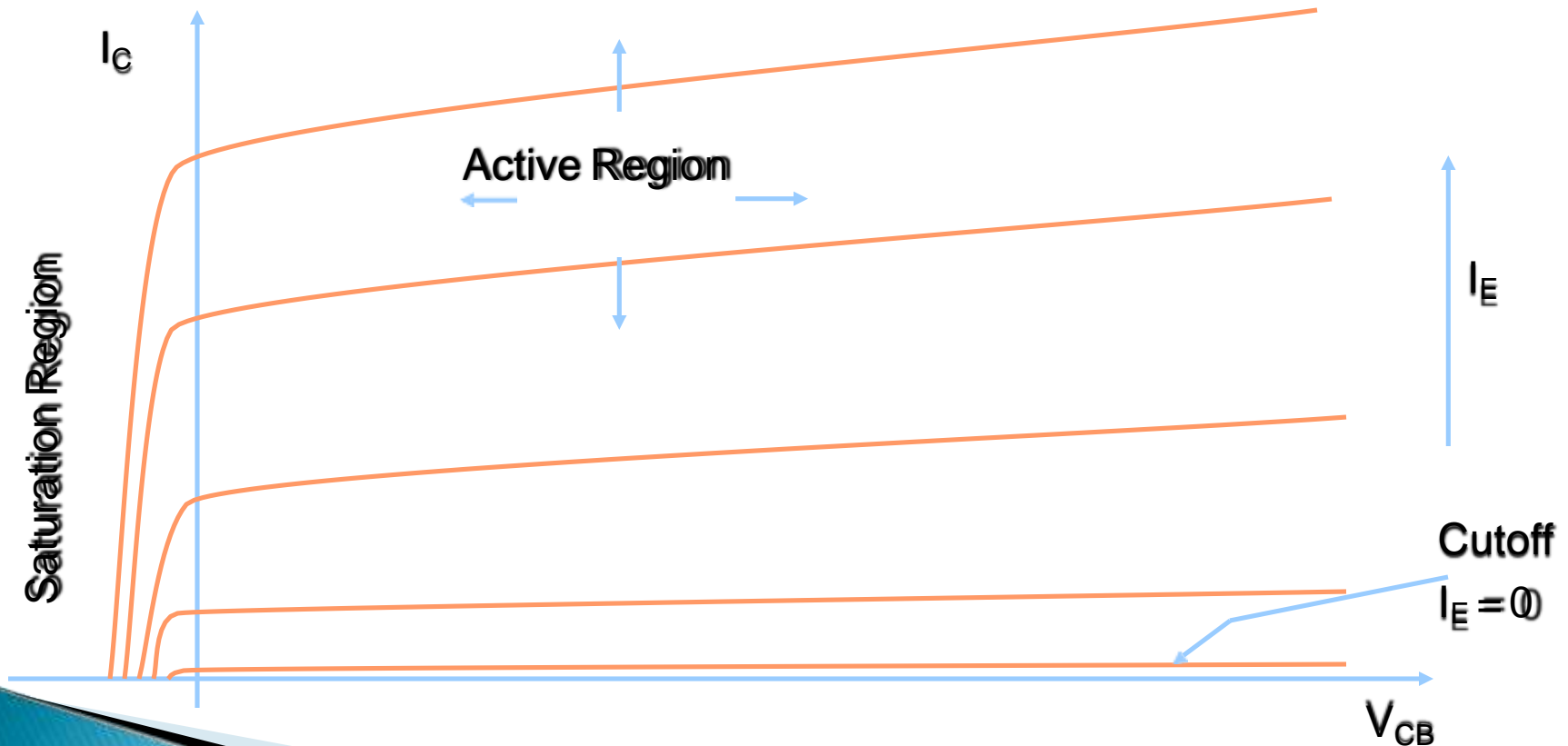

Common-Base

Circuit Diagram: NPN Transistor

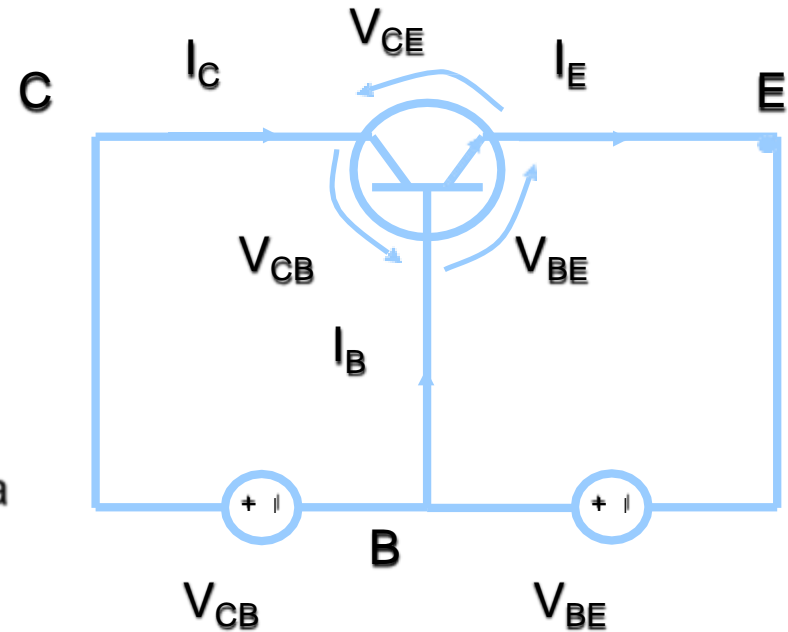


The Table Below lists assumptions that can be made for the attributes of the common-base biased circuit in the different regions of operation. Given for a Silicon NPN transistor.

Region of Operation	I_C	V_{CE}	V_{BE}	V_{CB}	C-B Bias	E-B Bias
Active	βI_B	$= V_{BE} + V_{CE}$	$\sim 0.7V$	$0V$	Rev.	Fwd.
Saturation	Max	$\sim 0V$	$\sim 0.7V$	$-0.7V < V_{CE} < 0$	Fwd.	Fwd.
Cutoff	~ 0	$= V_{BE} + V_{CE}$	$0V$	$0V$	Rev.	None / Rev.

Common-Emitter

Circuit Diagram

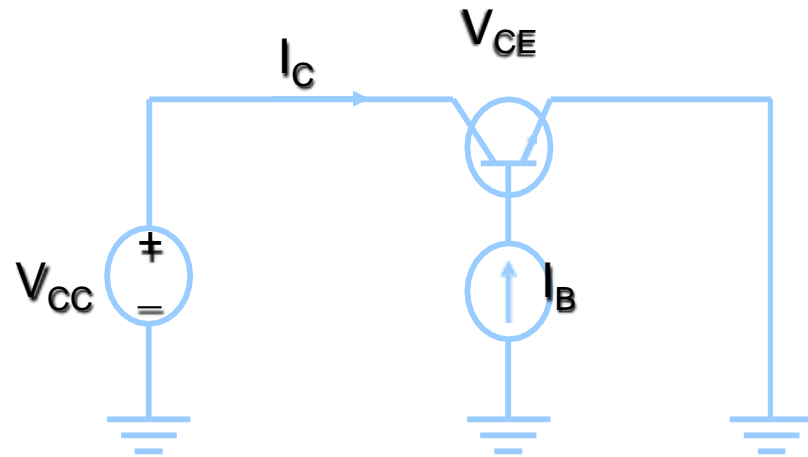

Region of Operation

Description

Active

Small base current controls a large collector current


Saturation

$V_{CE(sat)} \sim 0.2V$, V_{CE} increases with I_C

Cutoff

Achieved by reducing I_B to 0, Ideally, I_C will also equal 0


Collector-Current Curves

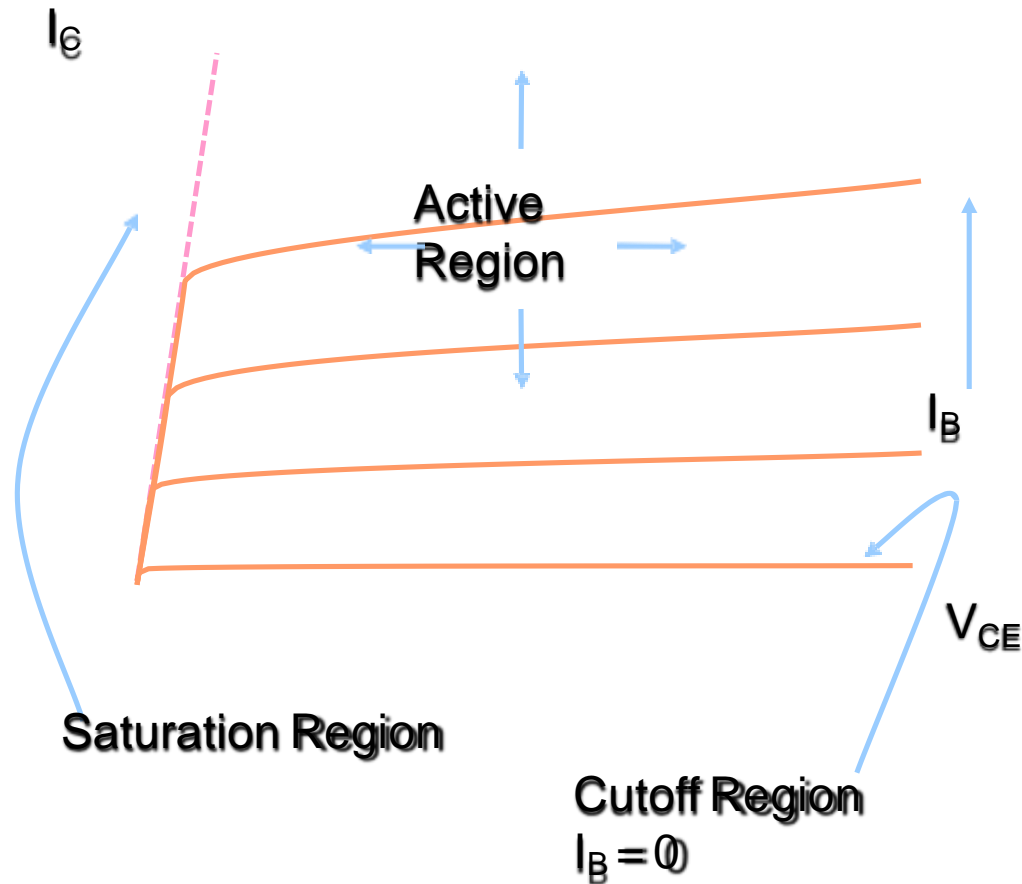

Common-Collector


The Common-Collector biasing circuit is basically equivalent to the common-emitter biased circuit except instead of looking at I_C as a function of V_{CE} and I_B we are looking at I_E . Also, since $\alpha \approx 1$, and $\alpha \equiv I_C / I_E$ that means $I_C \sim I_E$

Emitter-Current Curves

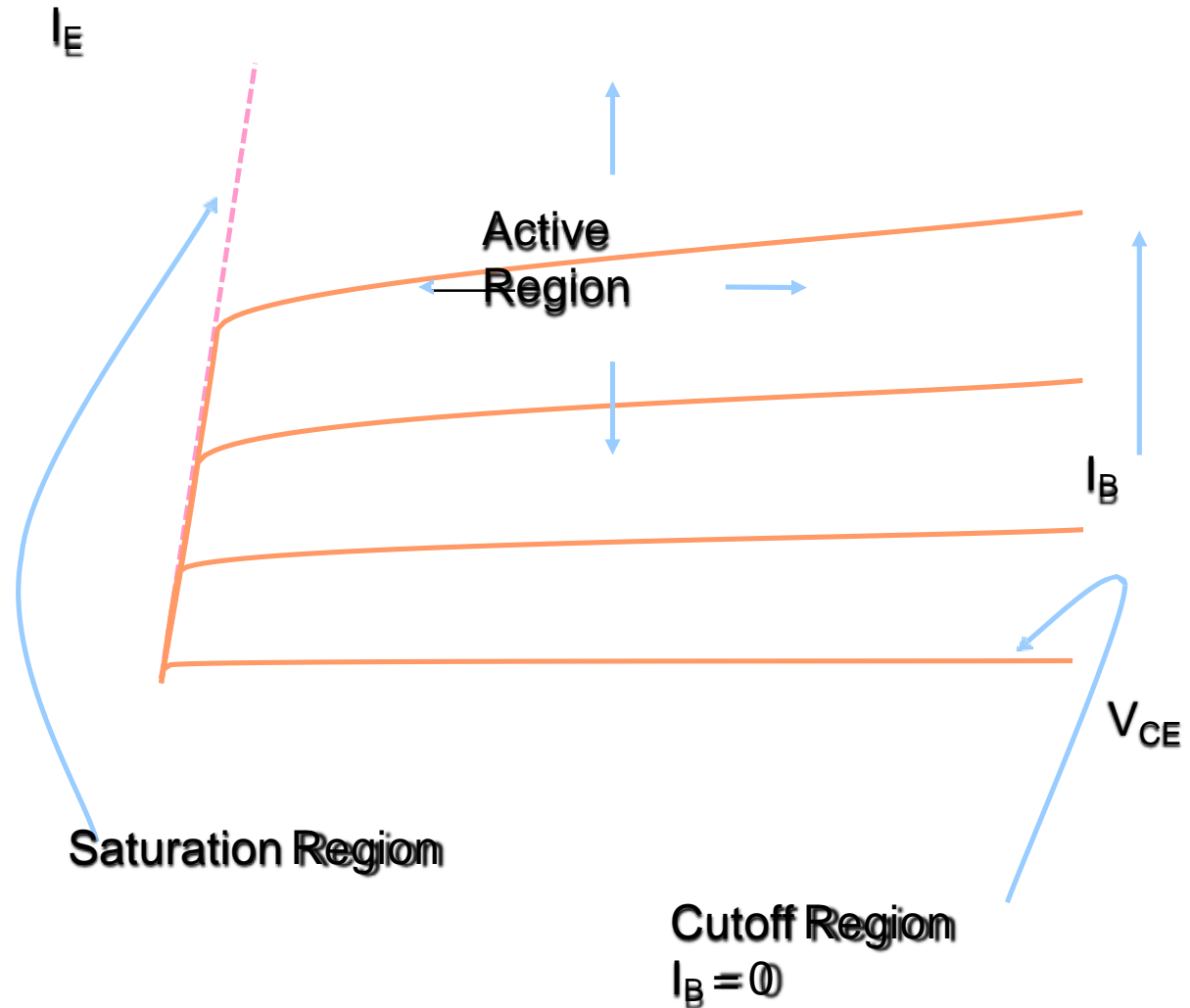

Eber-Moll BJT Model

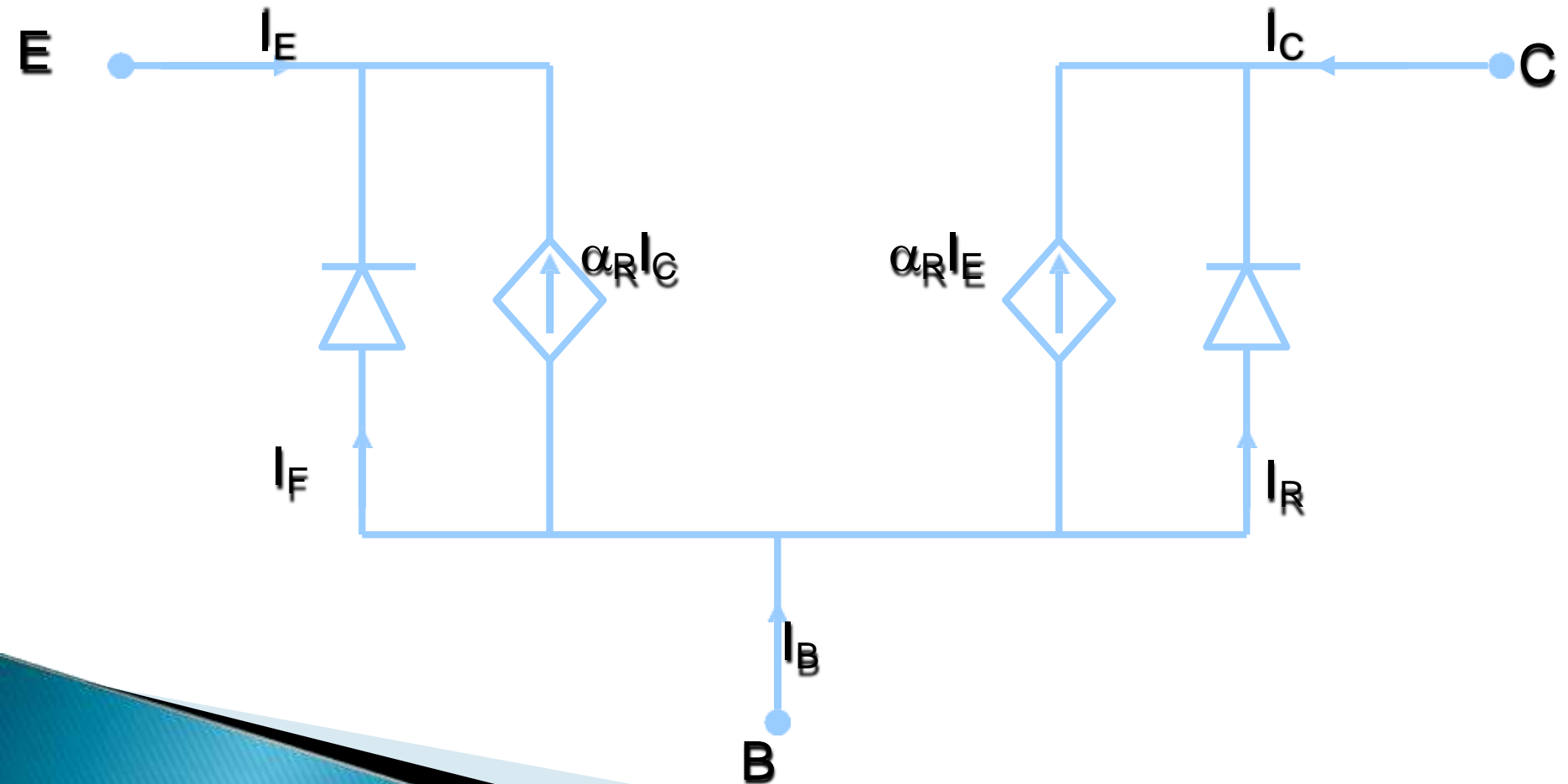The Eber-Moll Model for BJTs is fairly complex, but it is valid in all regions of BJT operation. The circuit diagram below shows all the components of the Eber-Moll Model:



Eber-Moll BJT Model

α_R = Common-base current gain (in forward active mode)

α_F = Common-base current gain (in inverse active mode)

I_{ES} = Reverse-Saturation Current of B-E Junction

I_{CS} = Reverse-Saturation Current of B-C Junction

$$I_C \equiv \alpha_F I_F - I_R \quad I_B \equiv I_E - I_C$$


$$I_E \equiv I_F - \alpha_R I_R$$

$$I_F \equiv I_{ES} [\exp(qV_{BE}/kT) - 1] \quad I_R \equiv I_{CS} [\exp(qV_{BC}/kT) - 1]$$

★ If I_{ES} & I_{CS} are not given, they can be determined using various BJT parameters.

Small Signal BJT Equivalent Circuit

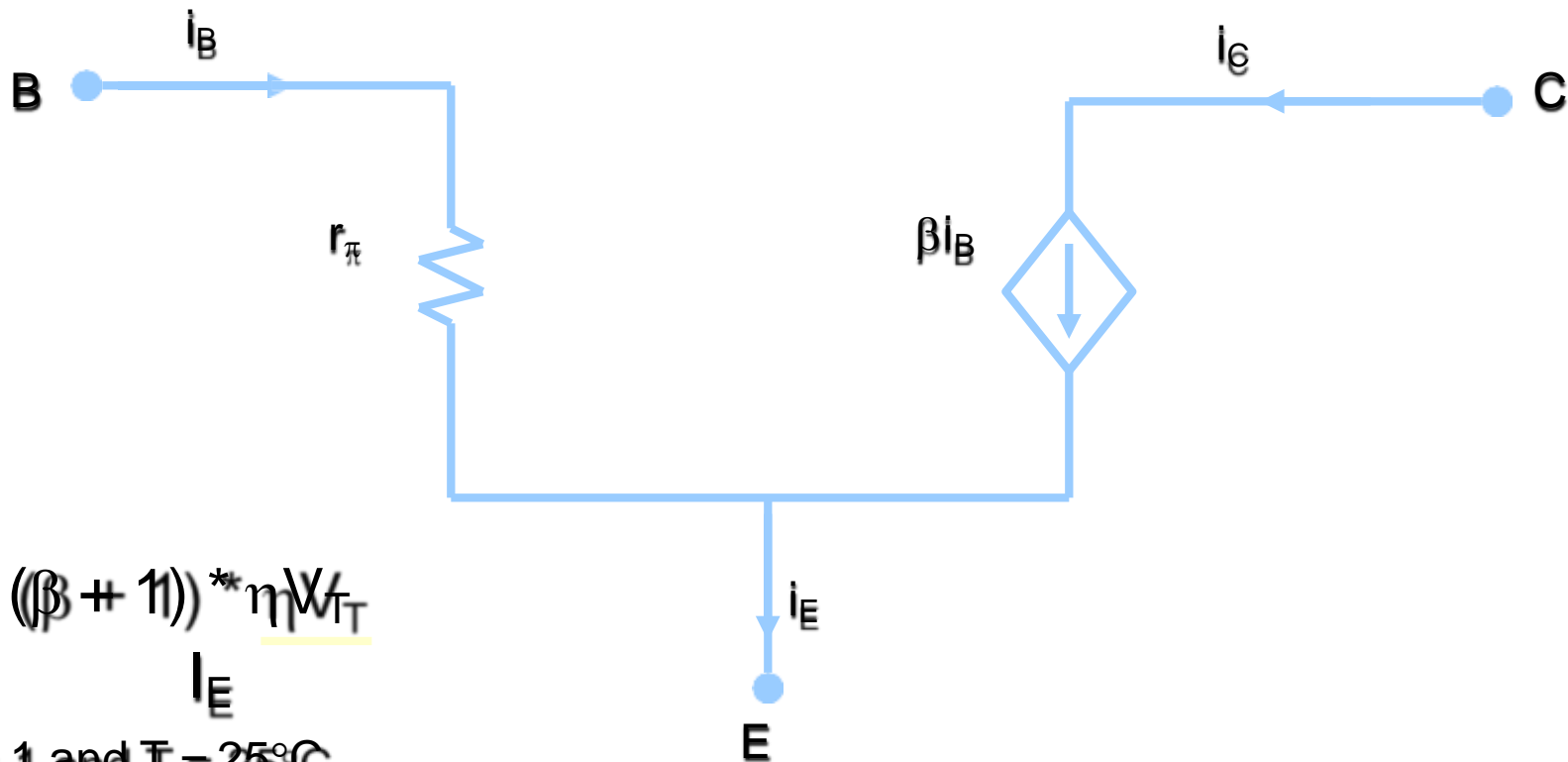The small-signal model can be used when the BJT is in the active region. The small-signal active-region model for a CB circuit is shown below:



$$r_{\pi} = (\beta + 1) * \eta \frac{V_T}{I_E}$$

$$I_E$$

@ $\eta = 1$ and $T = 25^\circ\text{C}$

$$r_{\pi} = (\beta + 1) * 0.026$$


$$I_E$$

Recall:

$$\beta = I_C / I_B$$

The Early Effect (Early Voltage)

Note: Common-Emitter Configuration

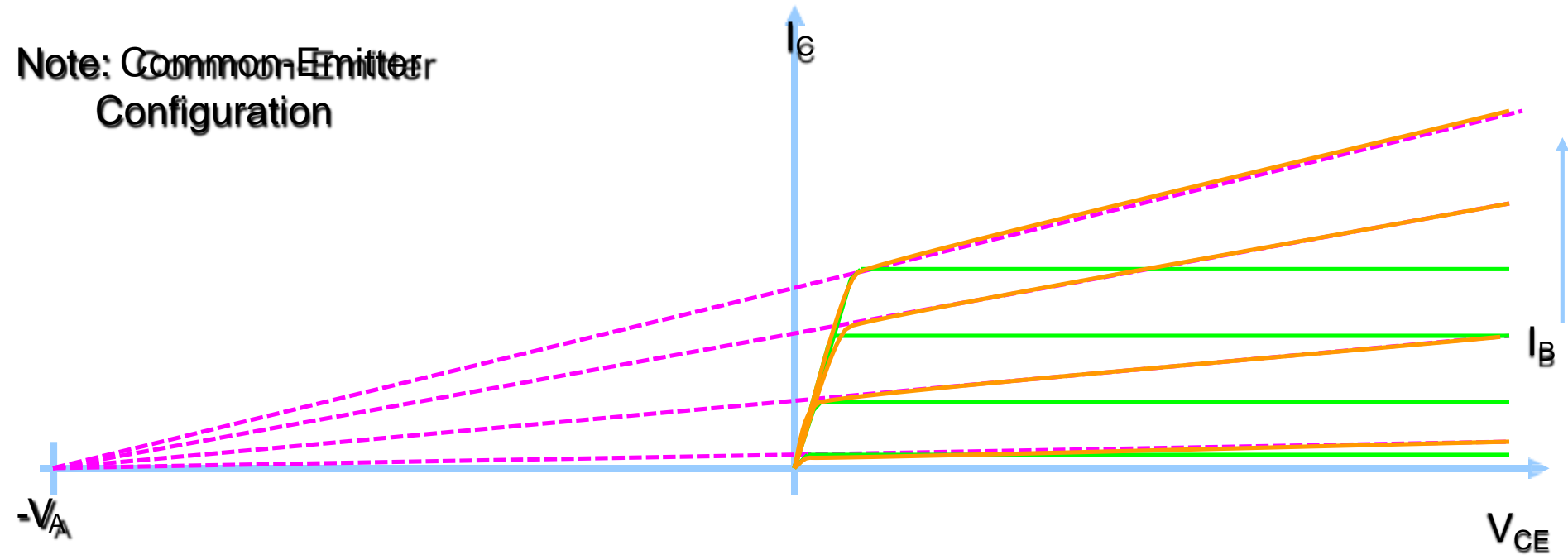

Green = Ideal I_C
 Orange = Actual $I_C (I_C')$

$$I_C' \equiv I_C \quad V_{CE} \neq 0$$

V_A




Early Effect Example

Given: The common-emitter circuit below with $I_B = 25 \mu A$, $V_{CE} = 15V$, $\beta = 100$ and $V_A = 80$.

Find: a) The ideal collector current
b) The actual collector current

Circuit Diagram

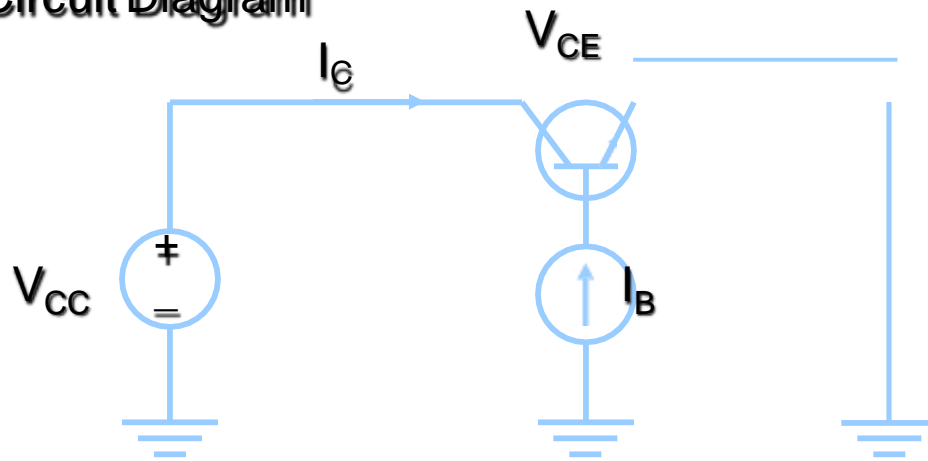

$$\beta = 100 = I_C / I_B$$

a)

$$I_C = 100 * I_B = 100 * (25 \times 10^{-6} A)$$

$$I_C = 2.5 mA$$

$$b) \quad I_C' = I_C \left(\frac{V_{CE} + 11}{V_A} \right) = 2.5 \times 10^{-3} \left(\frac{15 + 11}{80} \right) = 2.96 mA$$

$$I_C' = 2.96 mA$$