

UNIT –III

CHOPPER

S.SATHYAMOORTHY,
AP/EEE
NPRCET

Introduction

2

- ▶ Chopper is a static device.
- ▶ A variable dc voltage is obtained from a constant dc voltage source.
- ▶ Also known as dc-to-dc converter.
- ▶ Widely used for motor control.
- ▶ Also used in regenerative braking.
- ▶ Thyristor converter offers greater efficiency, faster response, lower maintenance, smaller size and smooth control.

Advantages:

3

- ▶ Regeneration
- ▶ Smooth acceleration
- ▶ Fast dynamic response

Applications:

4

- ▶ Trolley cars
- ▶ Used in electric cars
- ▶ Marine Hoists.
- ▶ Traction motor control

Types of choppers:

► Based on Output voltage:

- Step-Down chopper
- Step-up chopper
- Step Down/Up chopper

► Based on direction of Output V & I :

- Class –A,
- Class – B
- Class –C
- Class –D
- Class -E

► Based on Circuit Operation:

- First quadrant
- Two quadrant
- Four quadrant


► Based on Commutation method:

- Voltage commutation
- Current commutation
- Load commutation
- Impulse commutation


Based on output voltage Choppers:

- Step-down choppers.
 - In step down chopper output voltage is less than input voltage.
- Step-up choppers.
 - In step up chopper output voltage is more than input voltage.

Principle Of Step-down Chopper

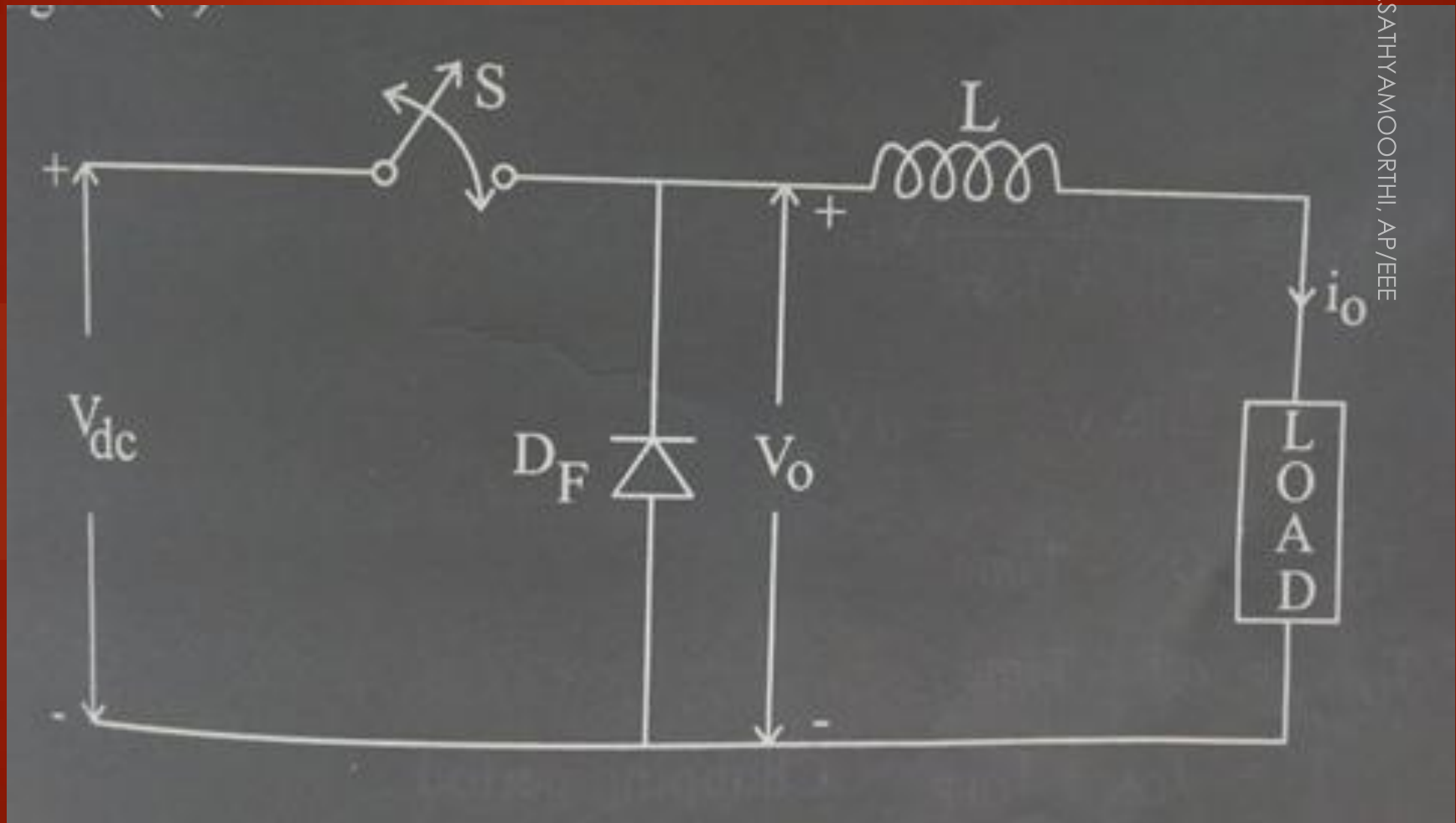

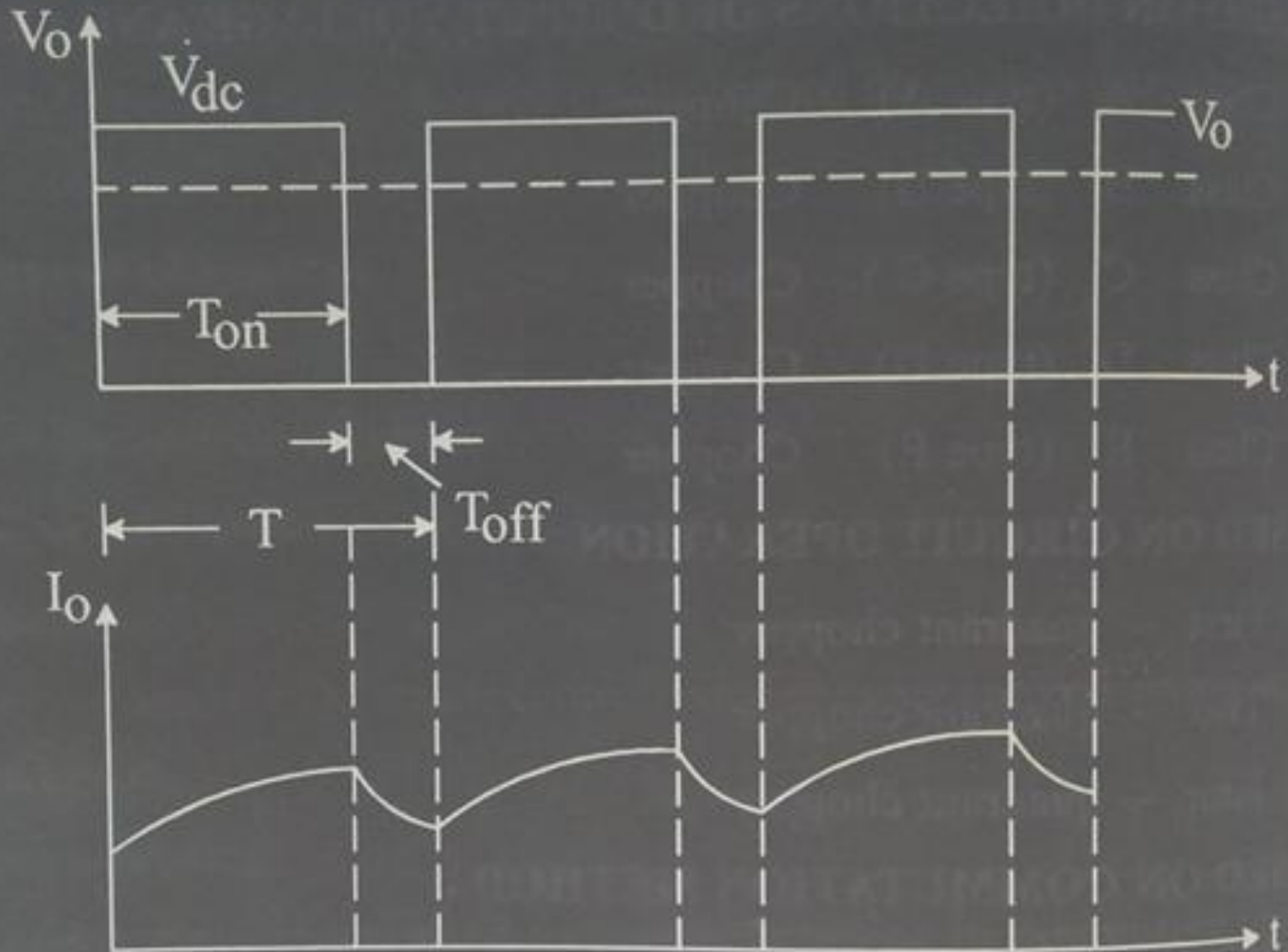- ▶ A step-down chopper with resistive load.
- ▶ The thyristor in the circuit acts as a switch.
- ▶ When thyristor is ON, supply voltage appears across the load
- ▶ When thyristor is OFF, the voltage across the load will be zero.



V_{dc} = Load voltage

I_{dc} = Load Current

T_{on} = Time interval for which SCR
conduct ON

T_{off} = Time interval for which SCR is
OFF

$T = T_{on} + T_{off}$

Average Output Voltage

$$V_{dc} = V \left(\frac{t_{ON}}{t_{ON} + t_{OFF}} \right)$$

$$V_{dc} = V \left(\frac{t_{ON}}{T} \right) = V.d$$

$$\text{but } \left(\frac{t_{ON}}{t} \right) = d = \text{duty cycle}$$

Average Output Current

13

$$I_{dc} = \frac{V_{dc}}{R}$$

$$I_{dc} = \frac{V}{R} \left(\frac{t_{ON}}{T} \right) = \frac{V}{R} d$$

RMS value of output voltage

$$V_o = \sqrt{\frac{1}{T} \int_0^{t_{ON}} v_o^2 dt}$$

But during t_{ON} , $v_o = V$

Therefore RMS output voltage

$$V_o = \sqrt{\frac{1}{T} \int_0^{t_{ON}} V^2 dt}$$

$$V_o = \sqrt{\frac{V^2}{T} t_{ON}} = \sqrt{\frac{t_{ON}}{T}} \cdot V$$

$$V_o = \sqrt{d} \cdot V$$

Output power $P_o = V_o I_o$

But $I_o = \frac{V_o}{R}$

\therefore Output power

$$P_o = \frac{V_o^2}{R}$$

$$P_o = \frac{dV^2}{R}$$

Effective input resistance of chopper


$$R_i = \frac{V}{I_{dc}}$$

$$R_i = \frac{R}{d}$$

The output voltage can be varied by varying the duty cycle.


Step-Up Chopper

17

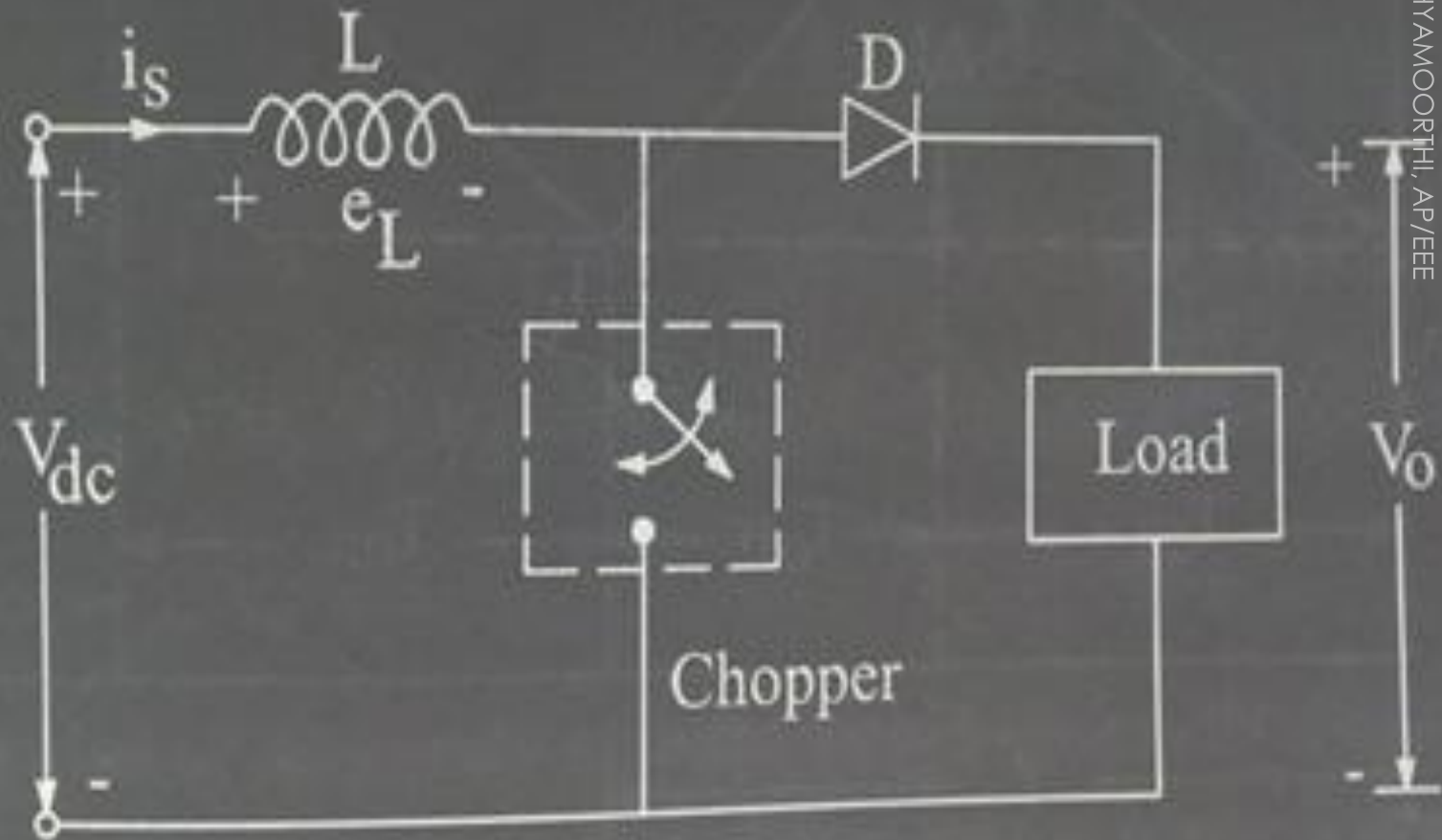



T_{on} Condition

18

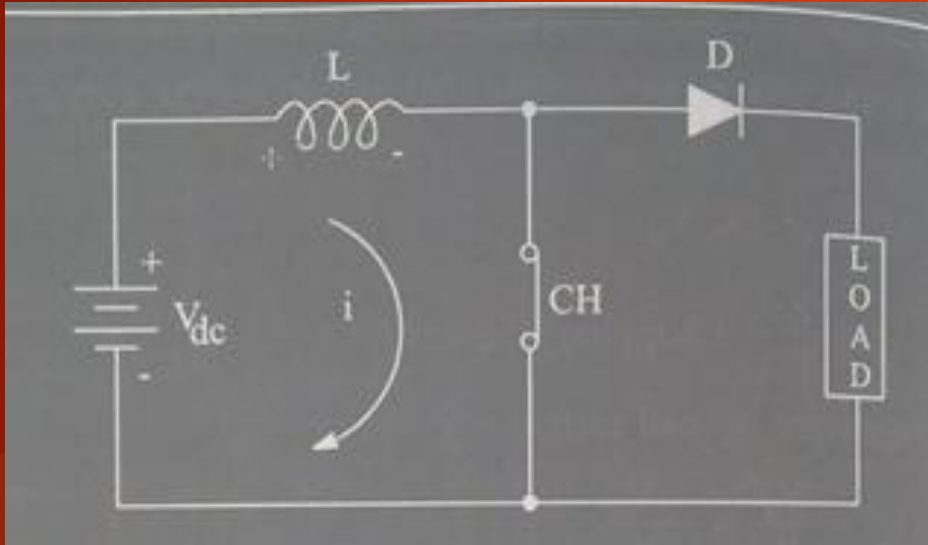

T_{off} Condition

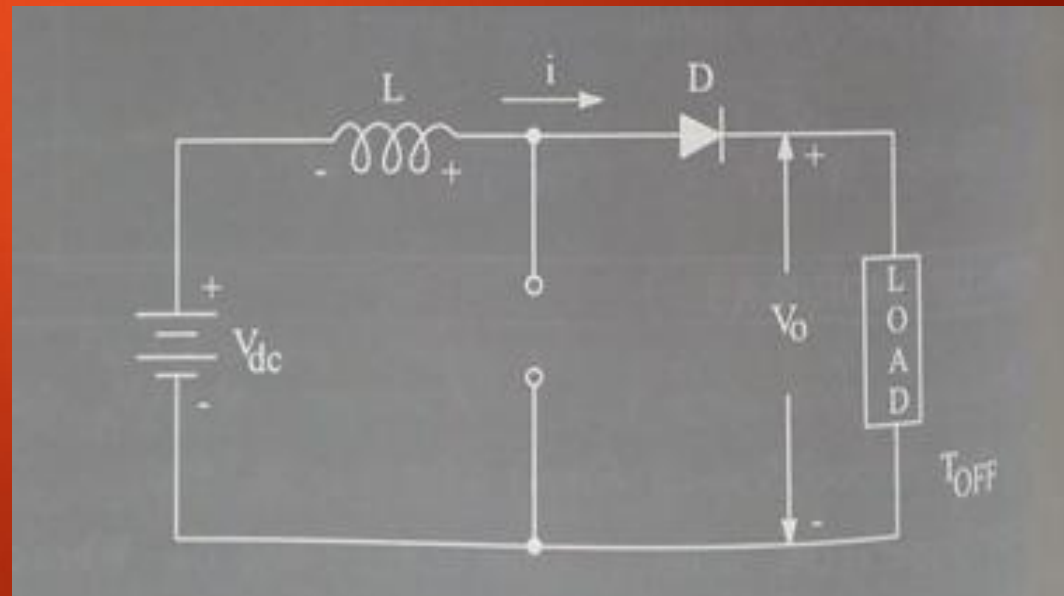

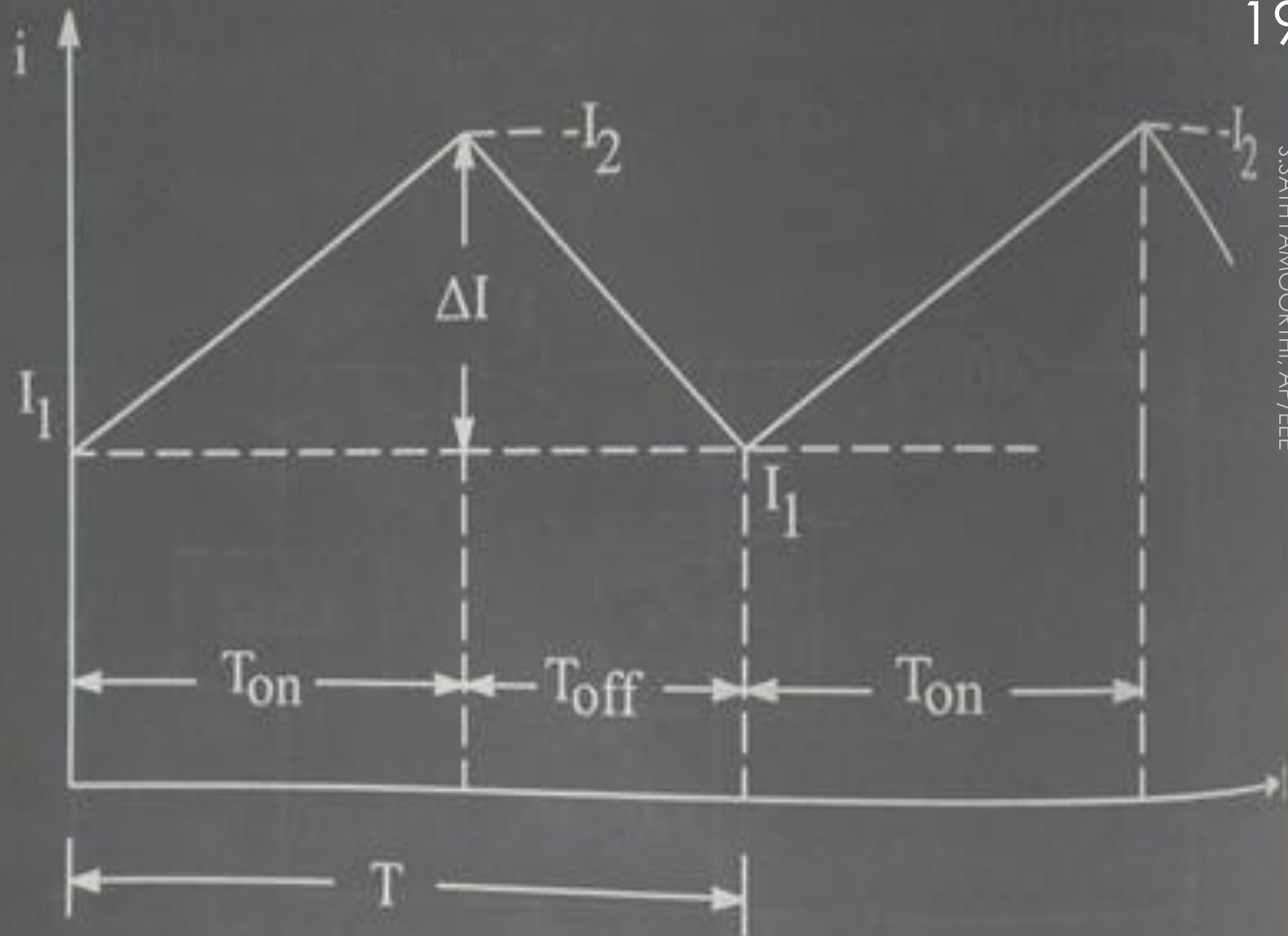



CHOOOPER CONFIGURATION

20

One Quadrant Operation:


First Quadrant Operation:

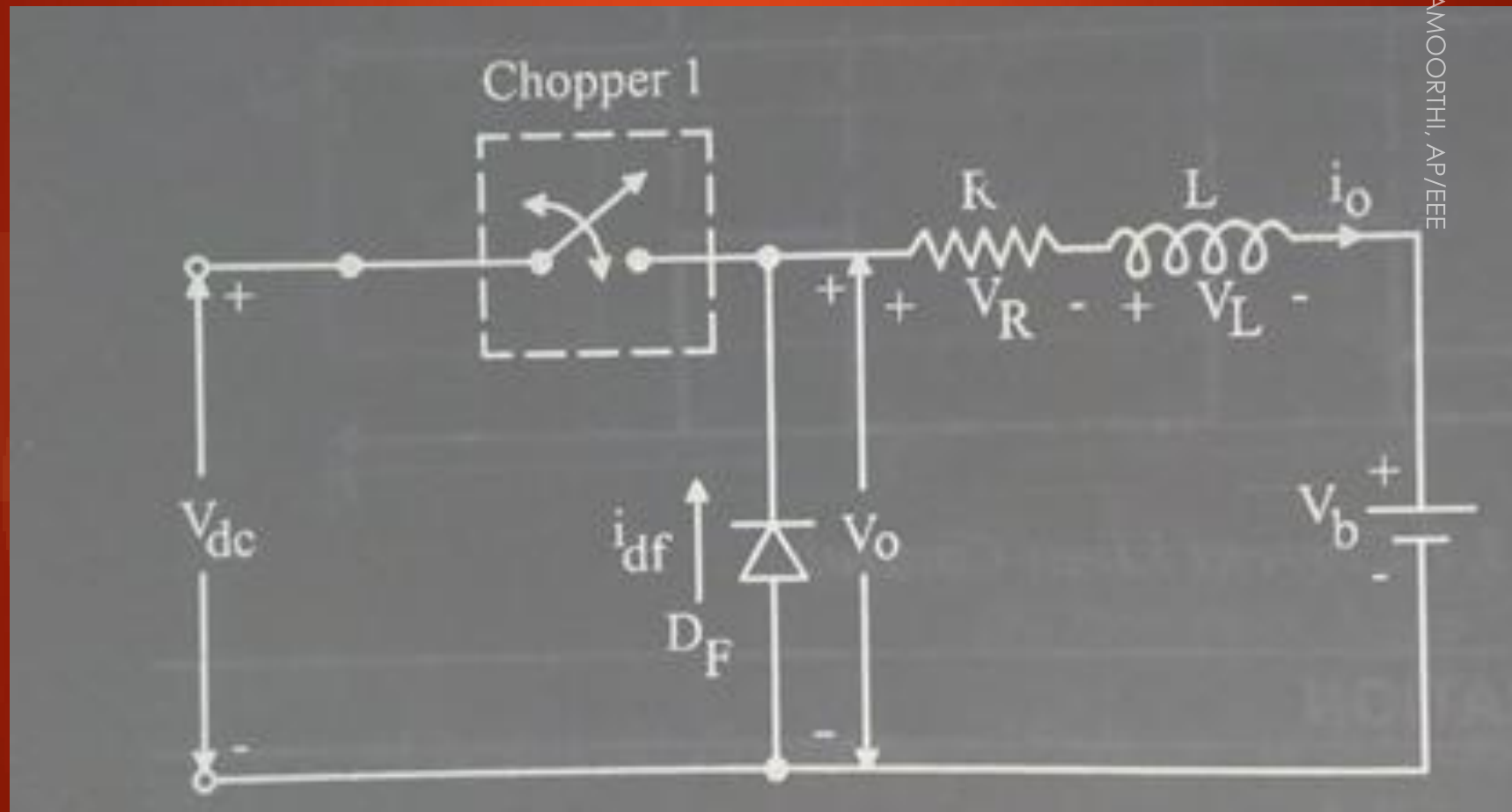


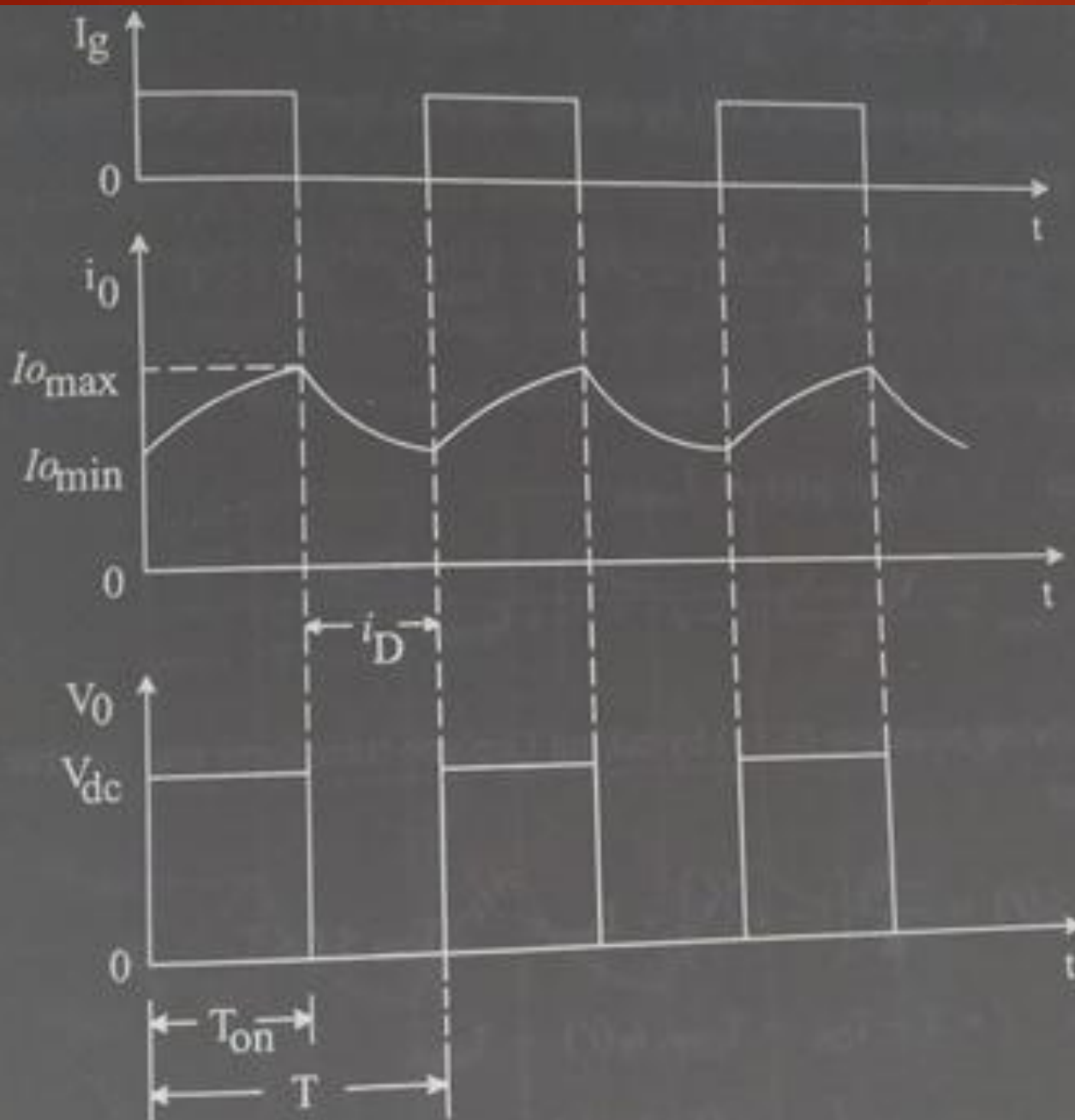

Second Quadrant Operation:

22

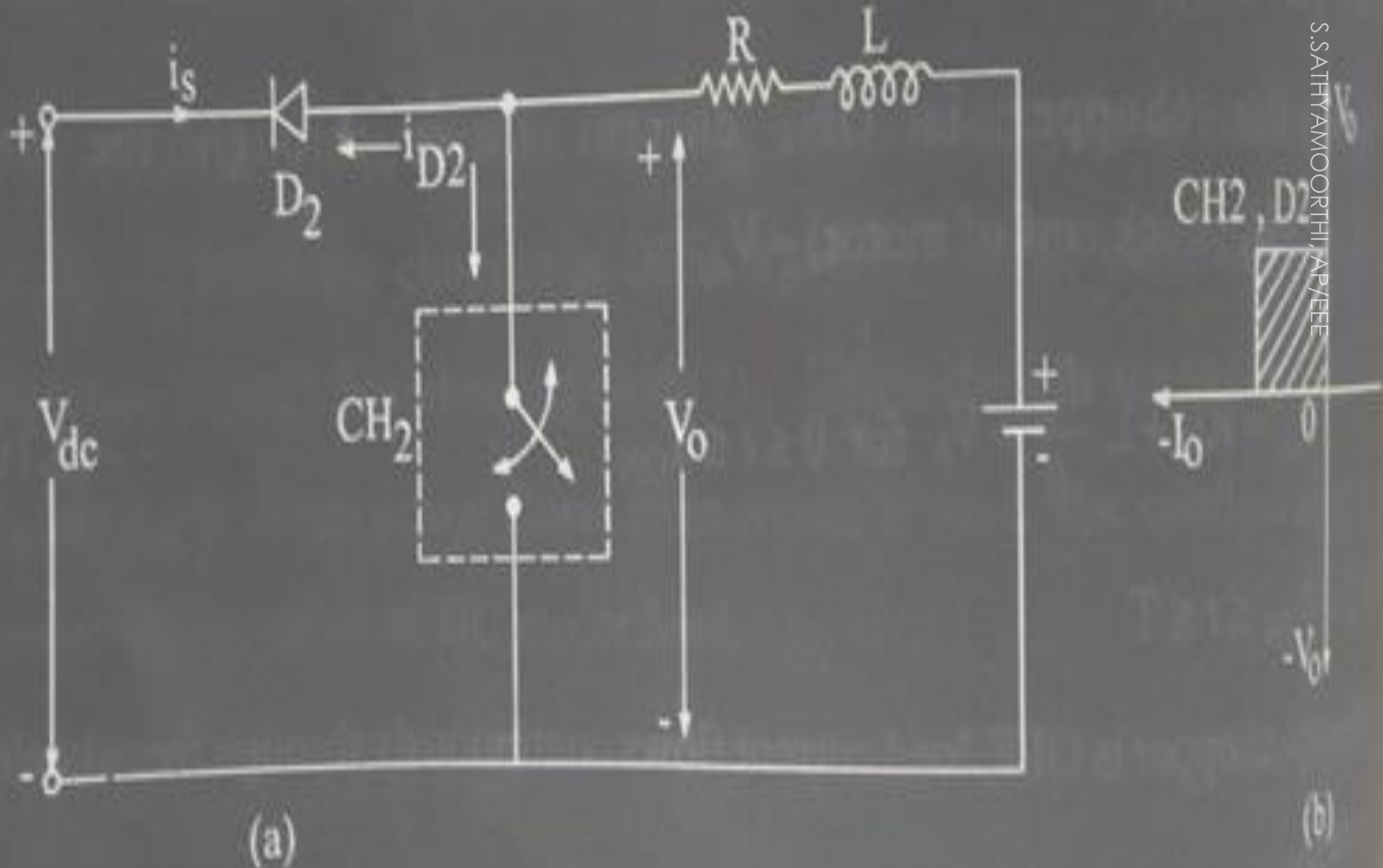


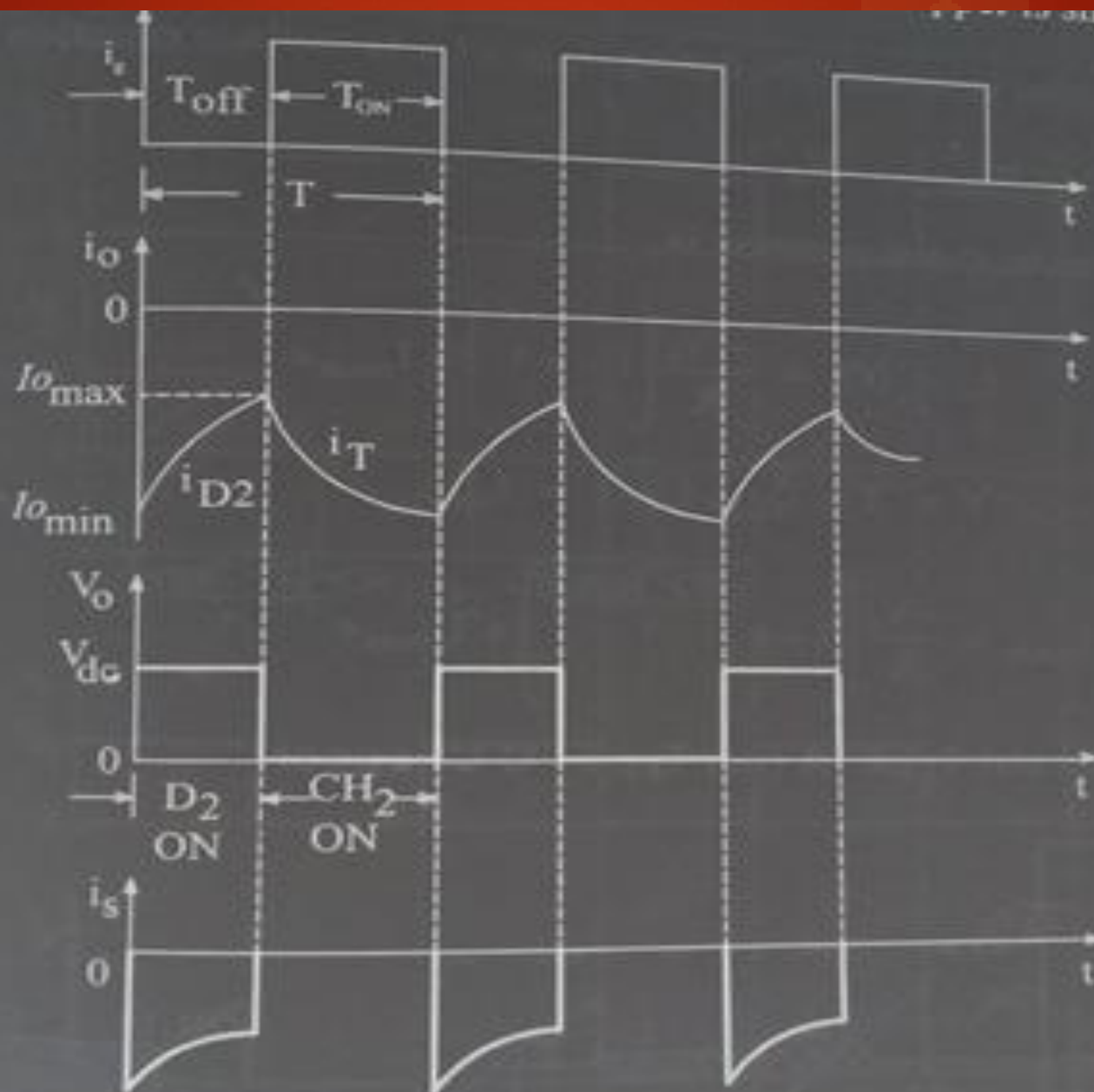


Two Quadrant Operation:

24


One & Two Quadrant Operation:

Class C Chopper:

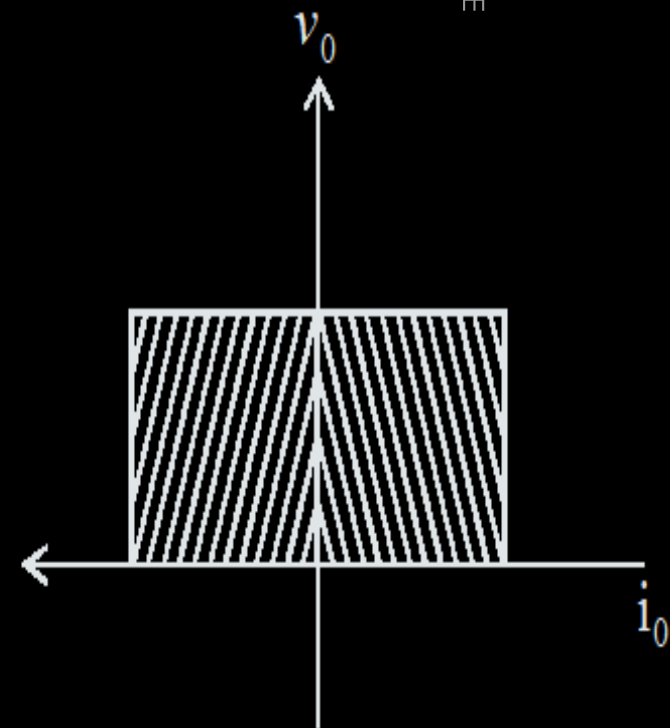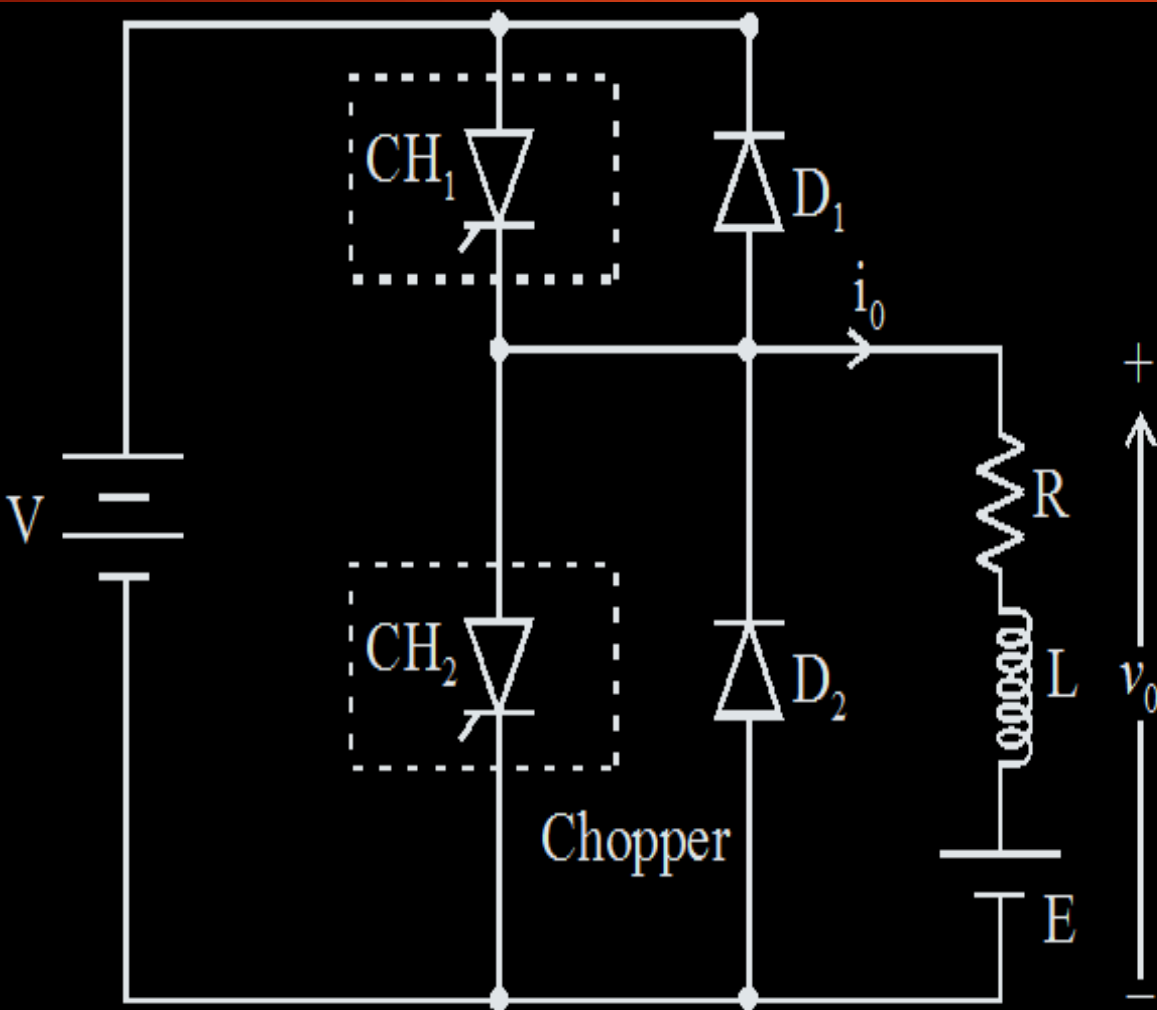


- ▶ Class C Chopper is a combination of Class A and Class B Choppers.
- ▶ For first quadrant operation, CH_1 is ON or D_2 conducts.
- ▶ For second quadrant operation, CH_2 is ON or D_1 conducts.
- ▶ When CH_1 is ON, the load current is positive.
- ▶ The output voltage is equal to 'V' & the load receives power from the source.
- ▶ When CH_1 is turned OFF, energy stored in inductance L forces current to flow through the diode D_2 and the output voltage is zero.

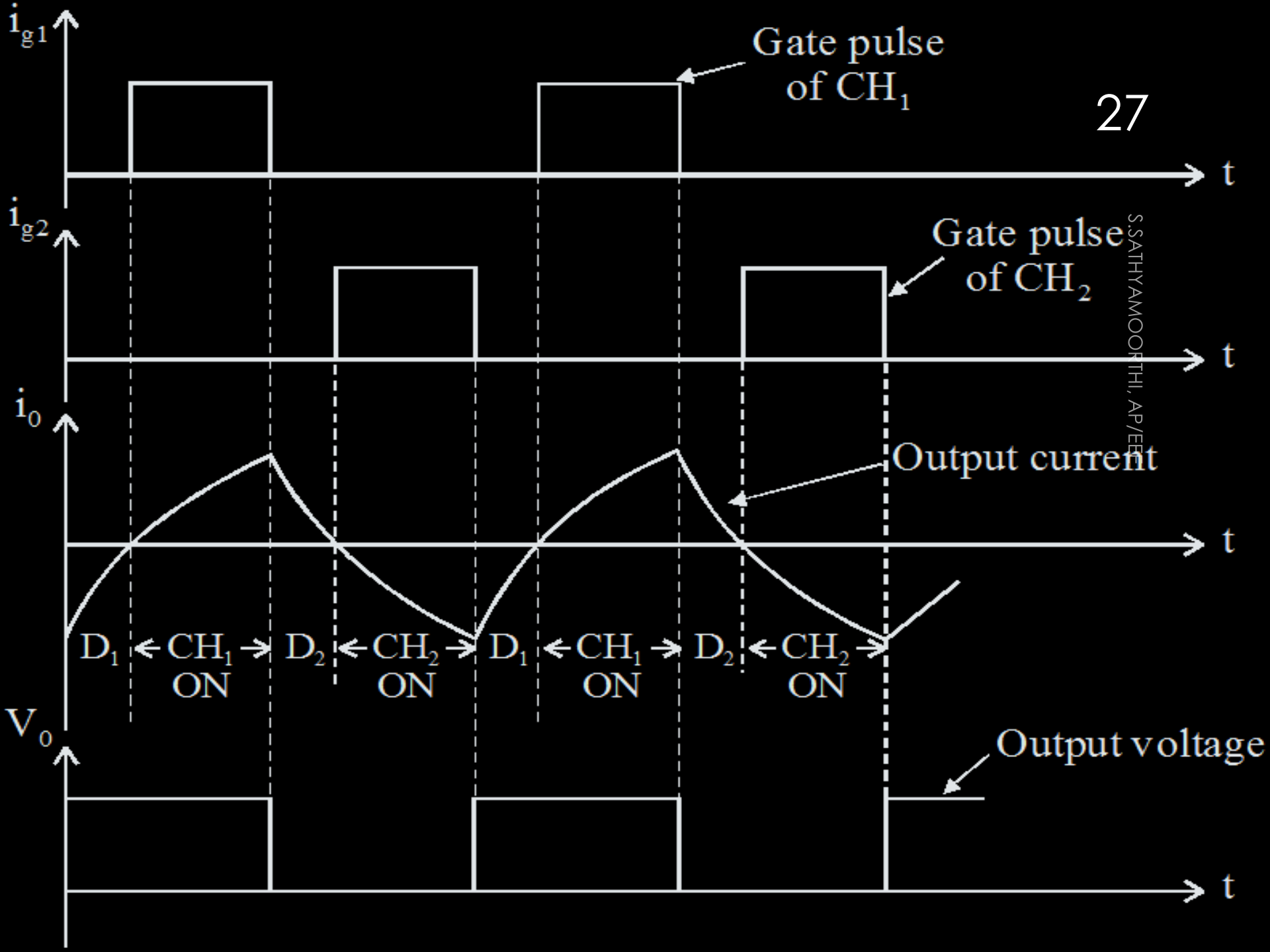- ▶ Current continues to flow in positive direction.
- ▶ When CH_2 is triggered, the voltage E forces current to flow in opposite direction through L and CH_2 .
- ▶ The output voltage is zero.
- ▶ On turning OFF CH_2 , the energy stored in the inductance drives current through diode D_1 and the supply
- ▶ Output voltage is V , the input current becomes negative and power flows from load to source.




Class D Chopper


28

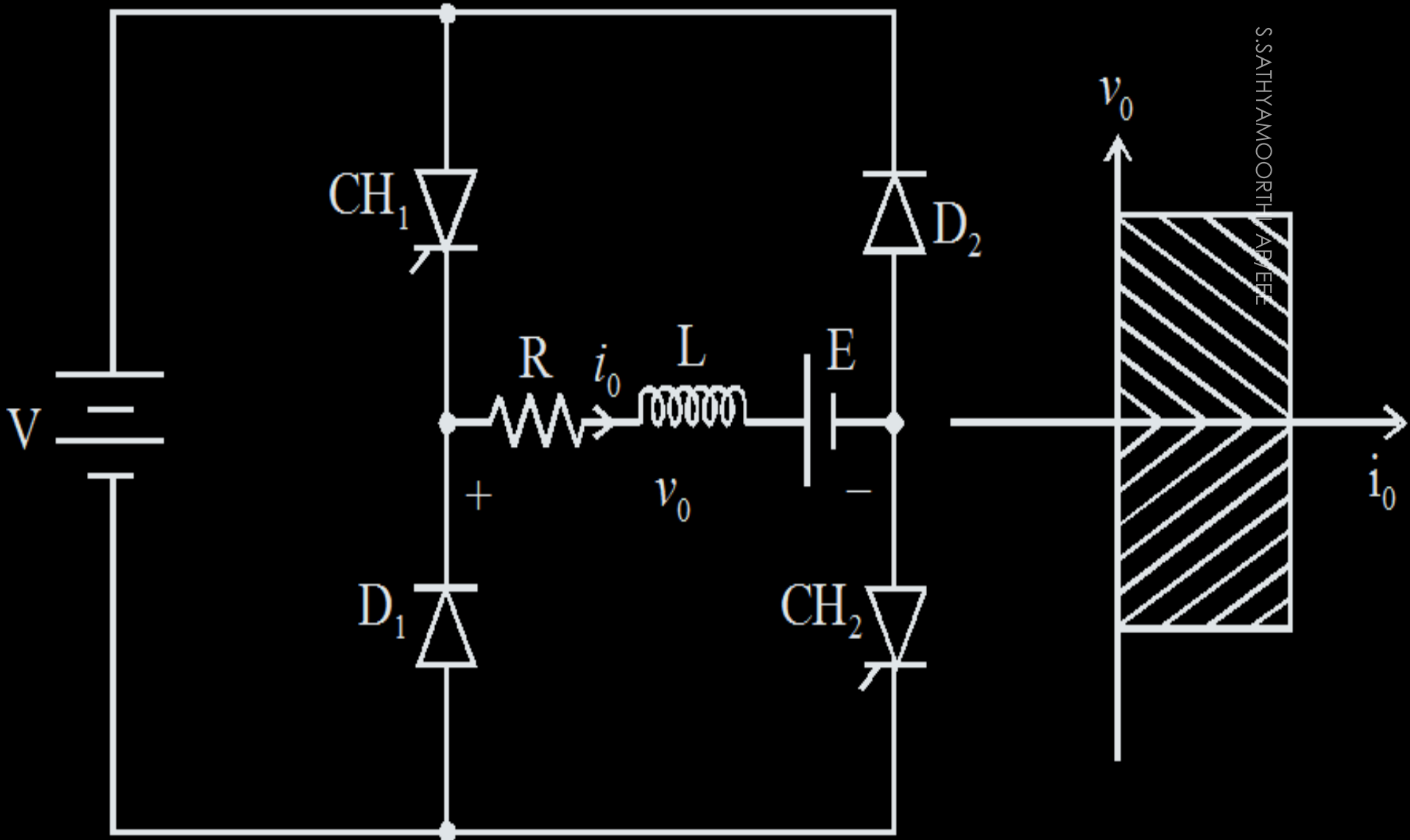

- ▶ Class D is a two quadrant chopper.
- ▶ When both CH_1 and CH_2 are triggered simultaneously, the output voltage $v_o = V$ and output current flows through the load.
- ▶ When CH_1 and CH_2 are turned OFF, the load current continues to flow in the same direction through load, D_1 and D_2 , due to the energy stored in the inductor L .
- ▶ Output voltage $v_o = -V$.

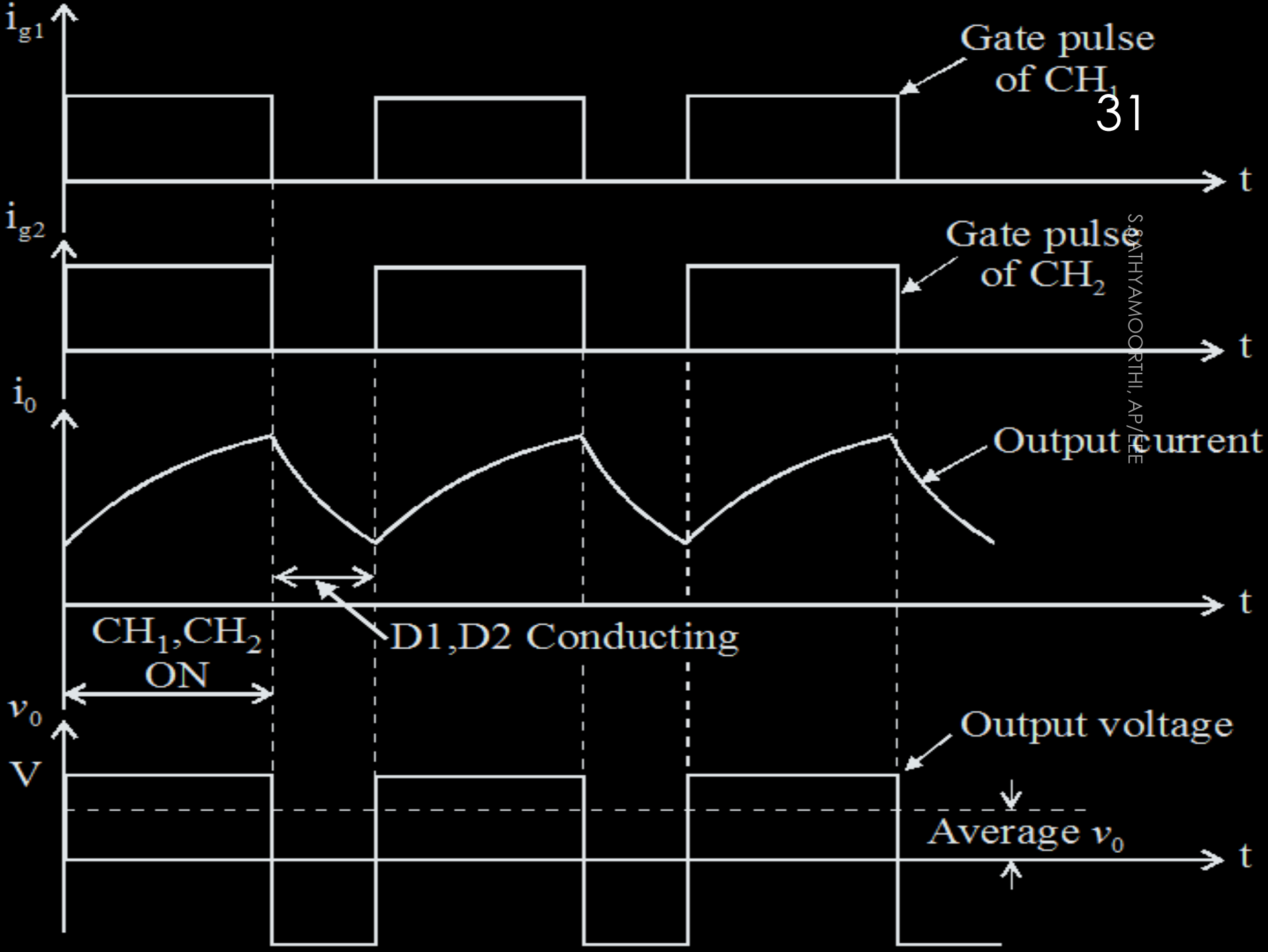
- ▶ Average load voltage is positive if chopper ON time is more than the OFF time
- ▶ Average output voltage becomes negative if $t_{ON} < t_{OFF}$.
- ▶ Hence the direction of load current is always positive but load voltage can be positive or negative.




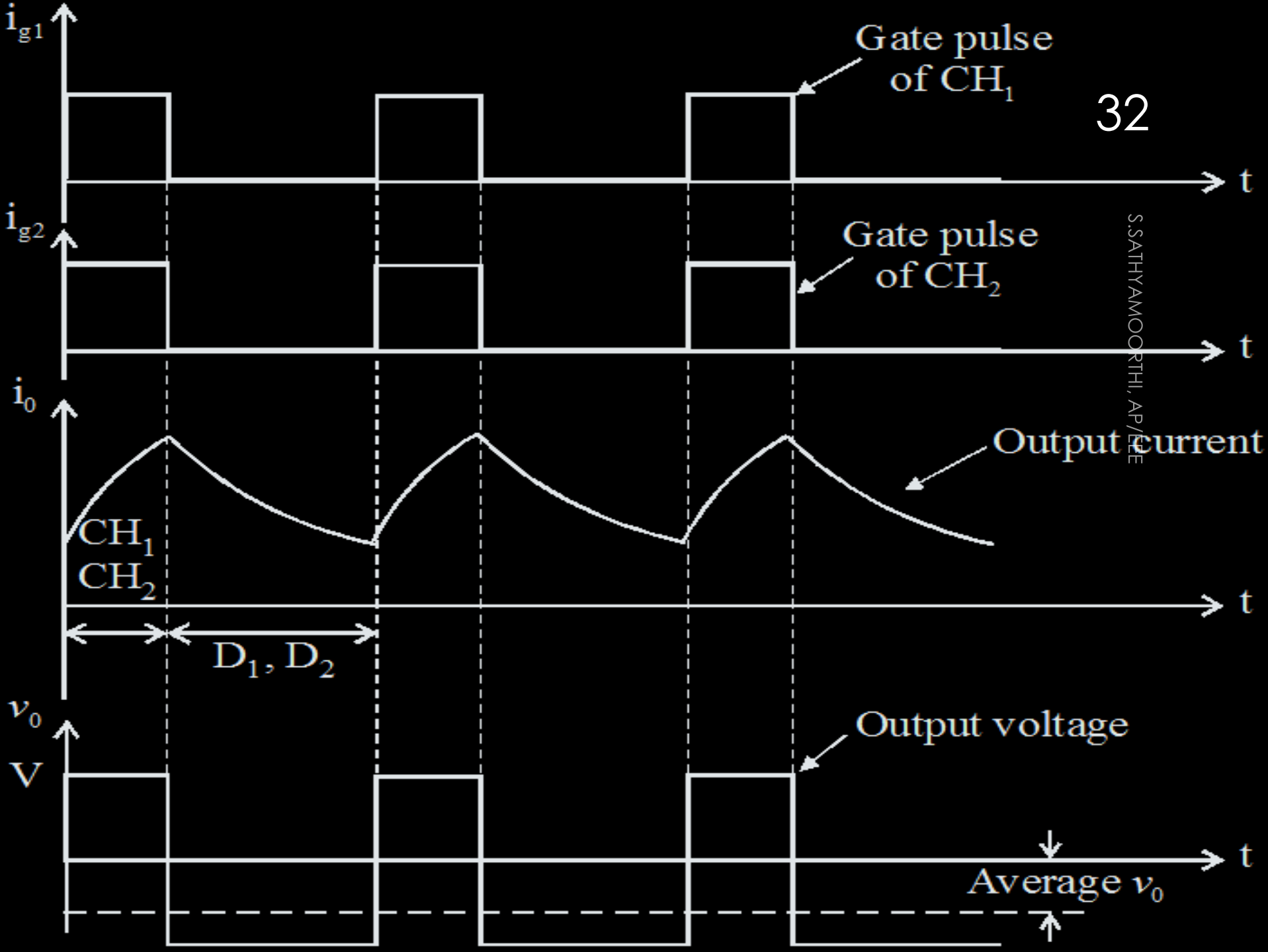

Class E Chopper

33

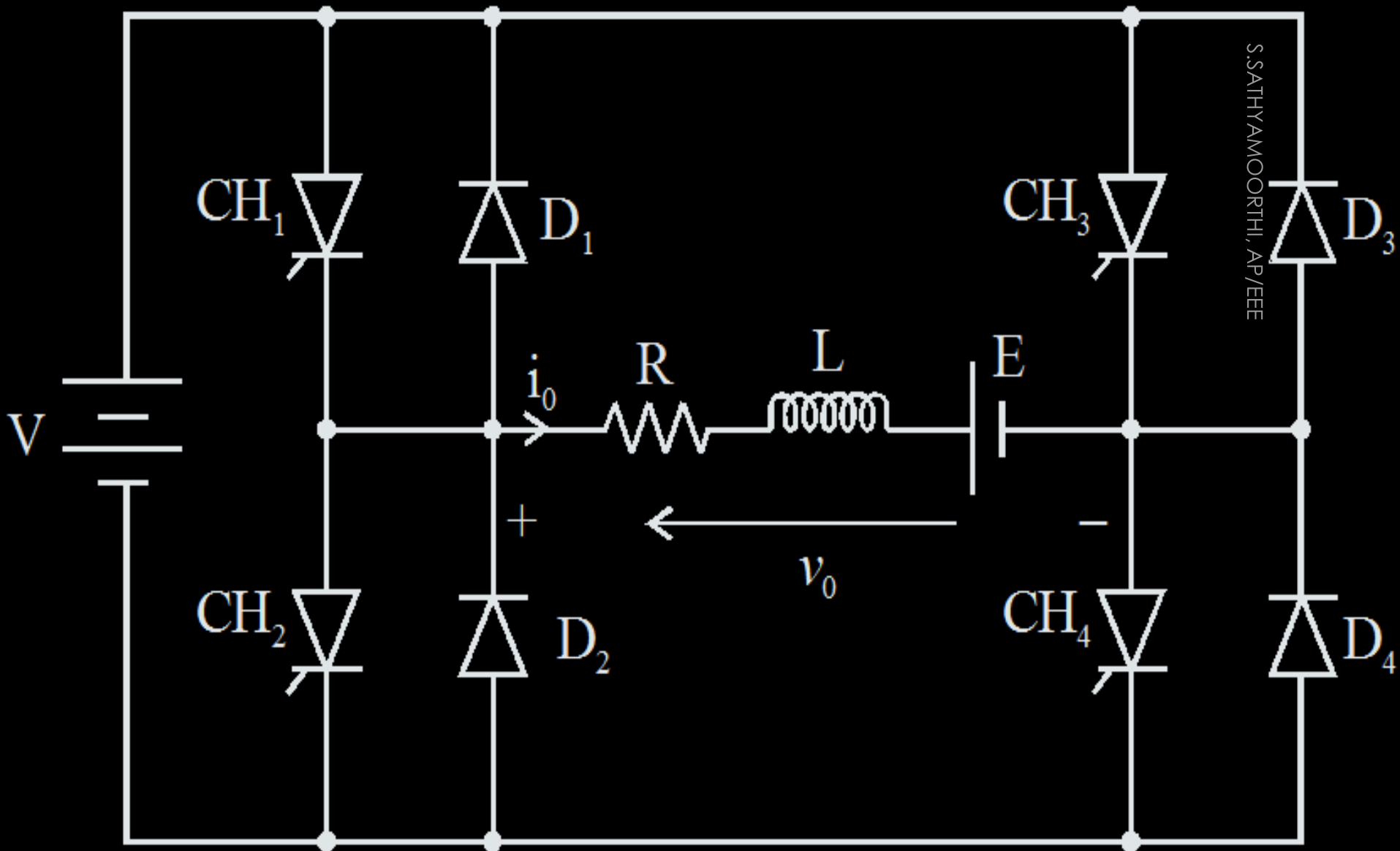

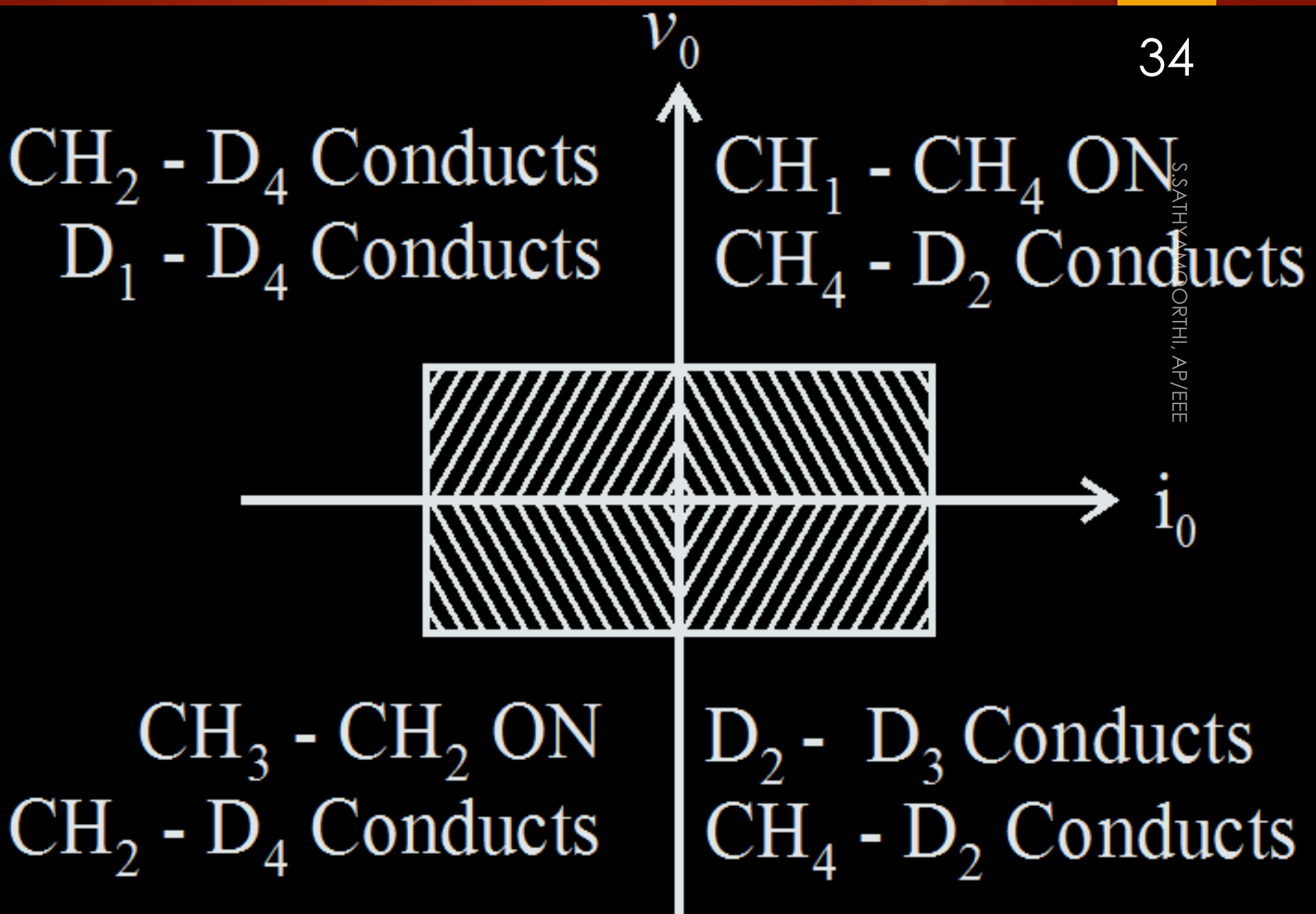


Fly Back Converter:

35


- ▶ Buck Converter (Step-Down)
- ▶ Boost Converter (Step-Up)
- ▶ Buck-Boost Converter
- ▶ Cuk Converter

Buck Converter:

36

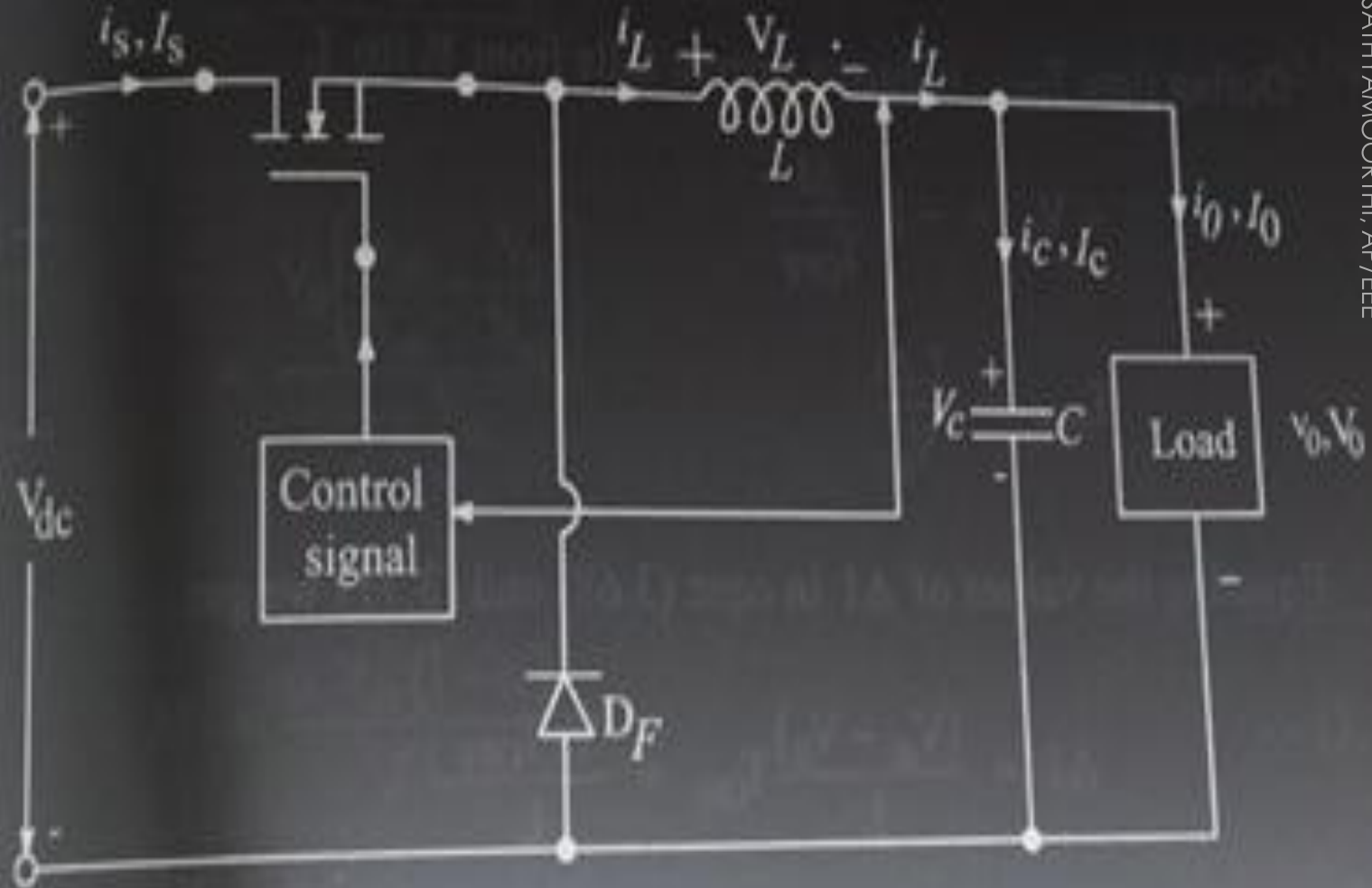


S.SATHYAMOORTHY, AP/EEE

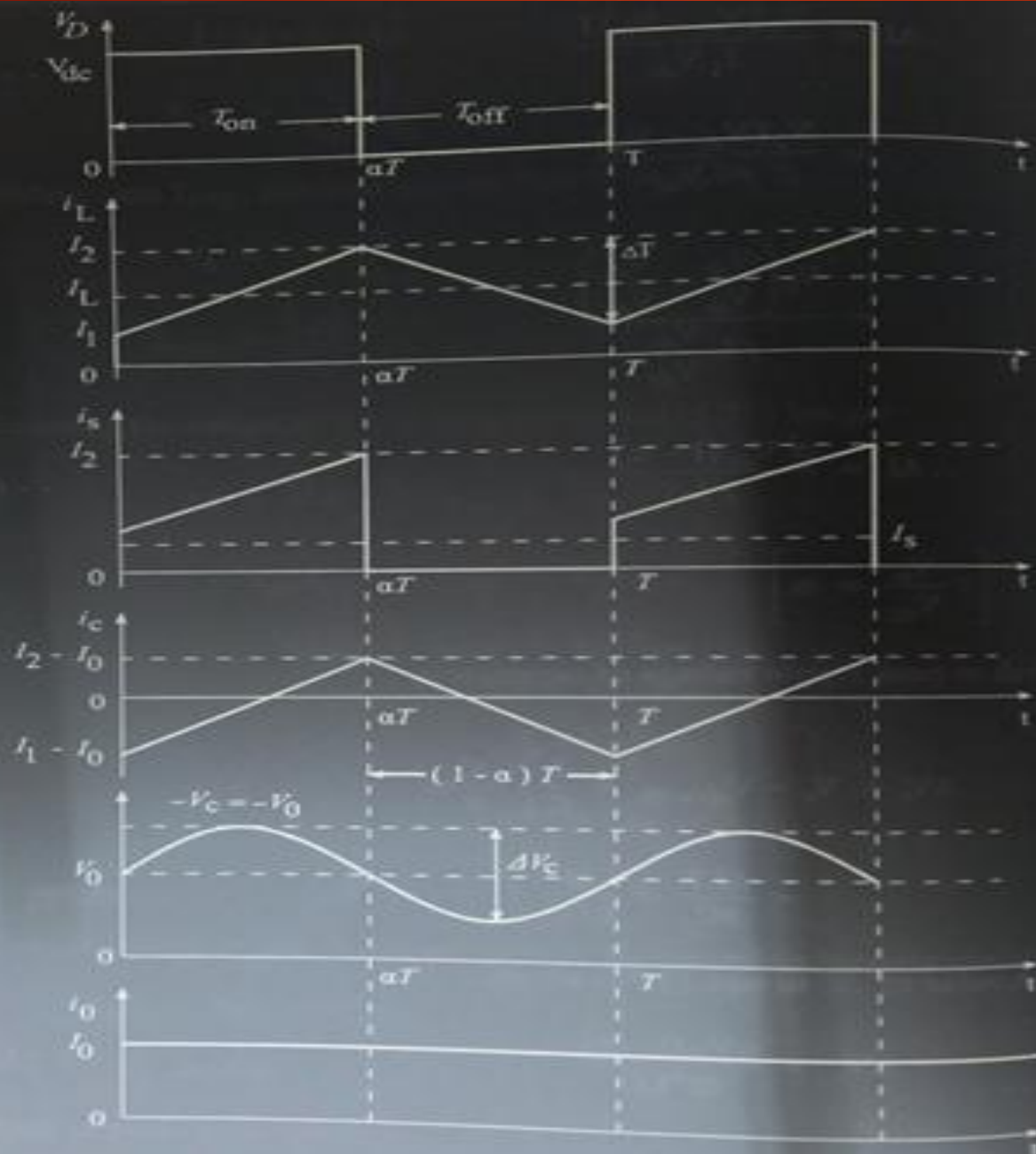


Boost Converter:

38

S.SATHYAMOORTHY, AP/EEE

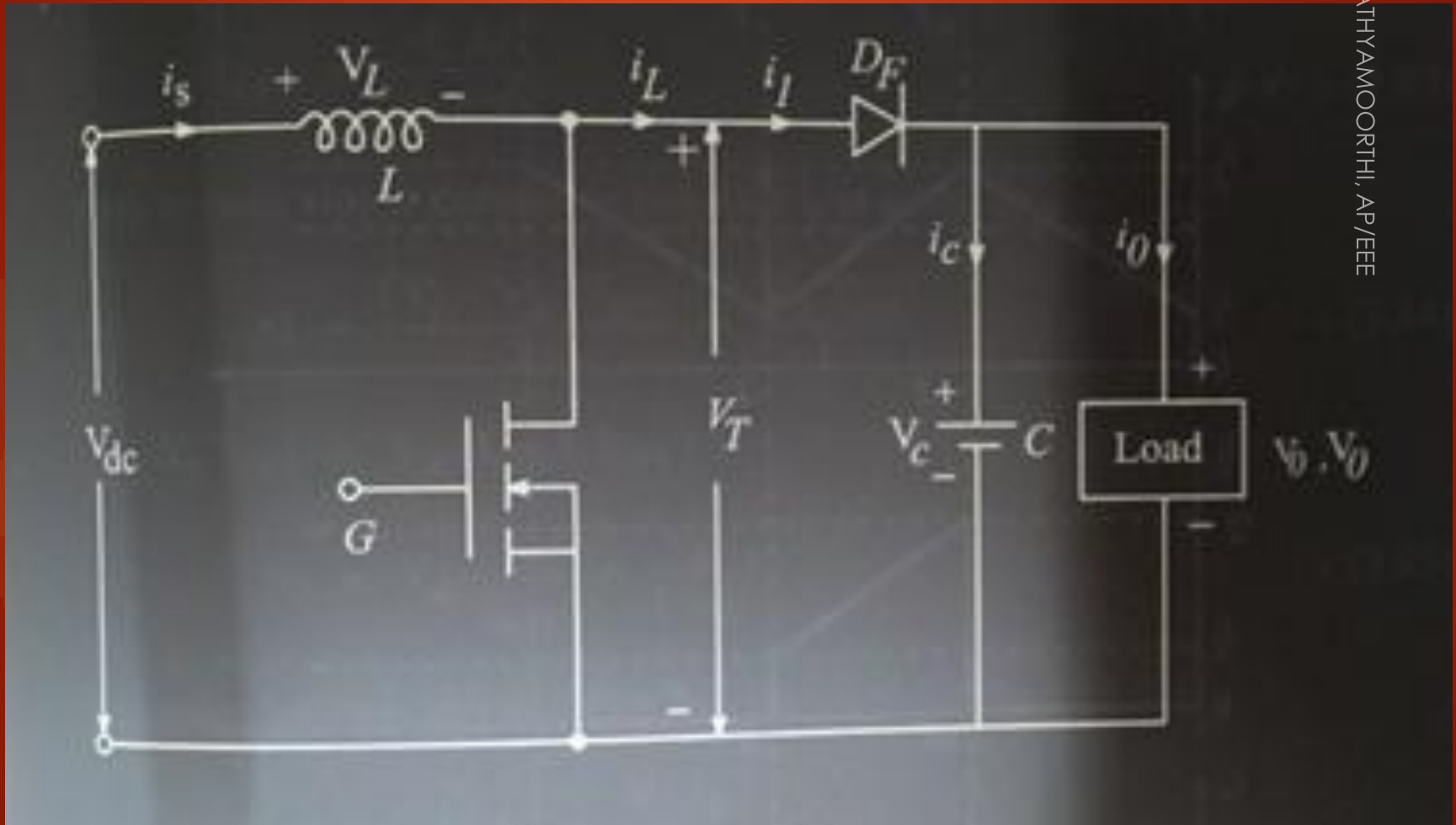


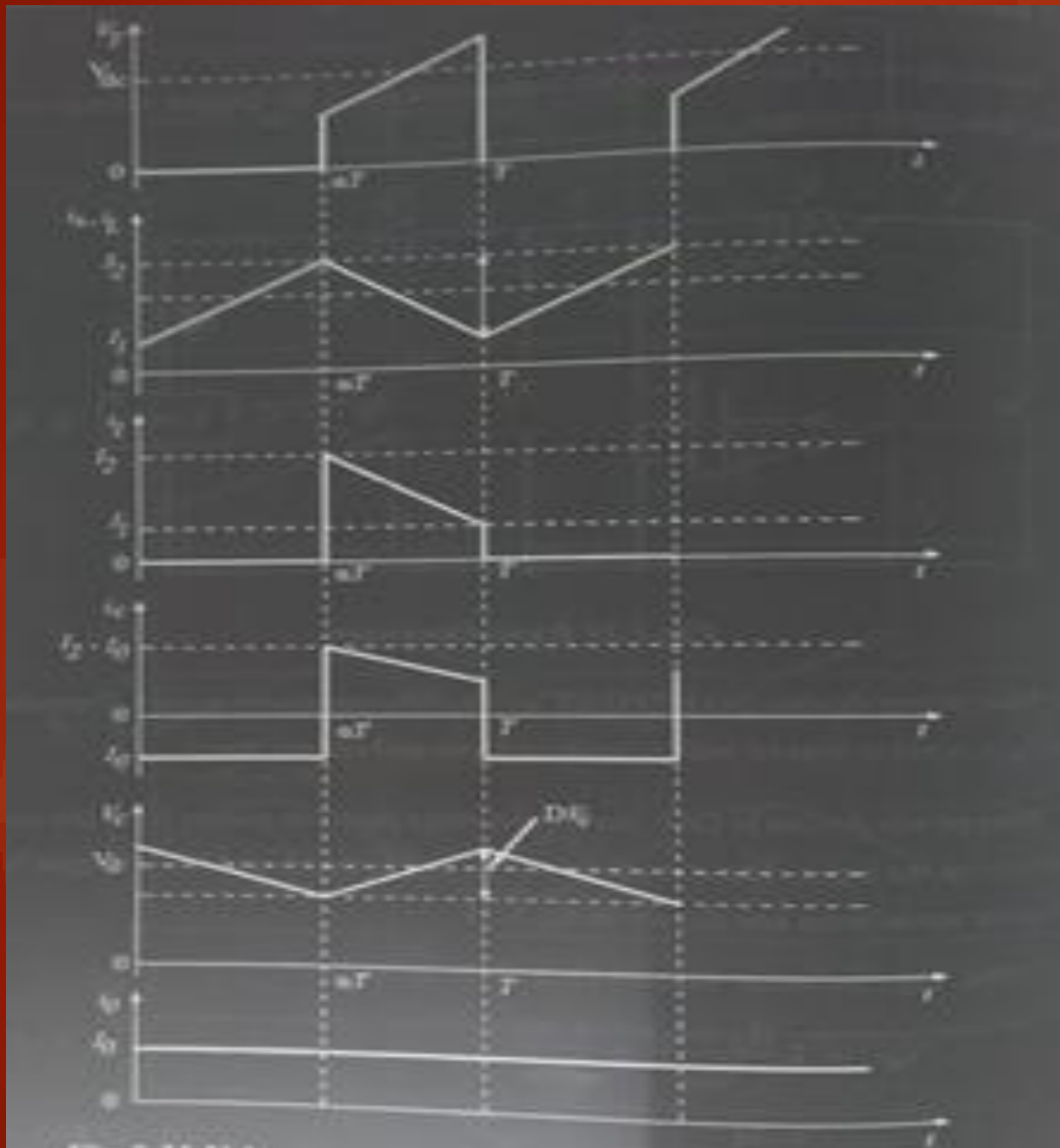

Buck- Boost Converter

40

S.SATHYAMOORTHY, AP/EEE

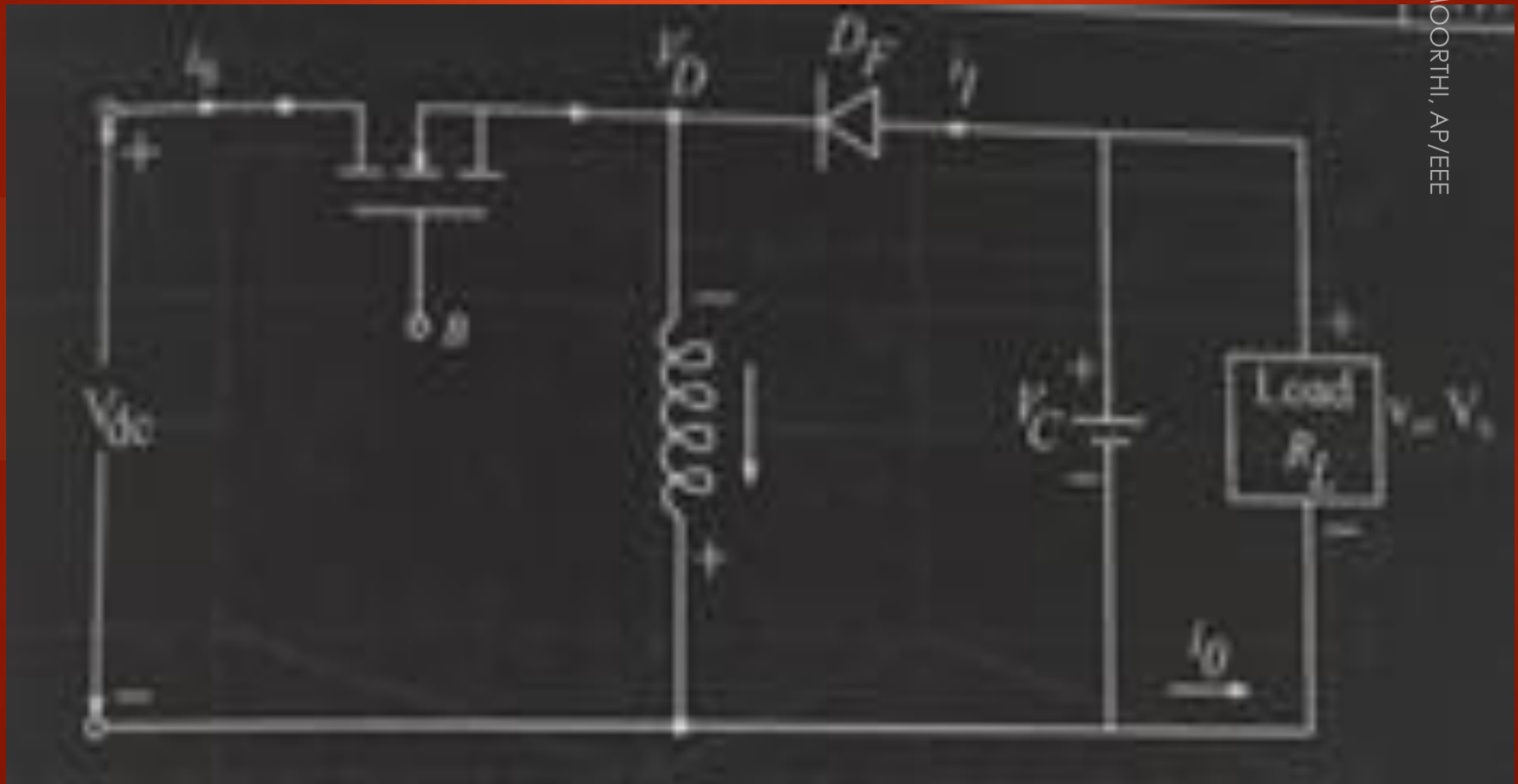

Cuk Converter:

41

